



Multiplexers

VLSI Systems
Assignment-6

PREPARED BY

Priyank Lohariwal

BCSE-IV

001710501055

Jadavpur University


Description

Designing the following multiplexers


1. 2x1 mux using gate level modelling
2. 4x1 mux using gate level modelling
3. 8x1 mux using 4x1 and 2x1 multiplexers
4. 16x1 mux using 8x1 and 2x1 multiplexers
5. 16x1 mux using 4x1 multiplexers

2x1 Multiplexer

Block Diagram

 

Circuit Diagram

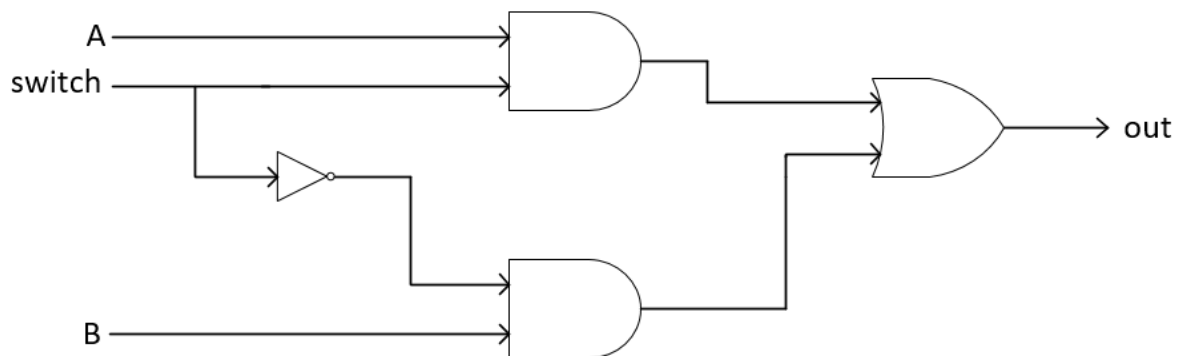

Truth Table

Inputs			Output
s	A	B	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Code

```
architecture Behavioral of mux2x1 is
    signal a,b: std_logic;
begin
    a <= (X(0) nand s);
    b <= (X(1) nand (not s));


    Y <= a nand b;
end Behavioral;
```

4x1 Multiplexer

Block Diagram

 

Circuit Diagram

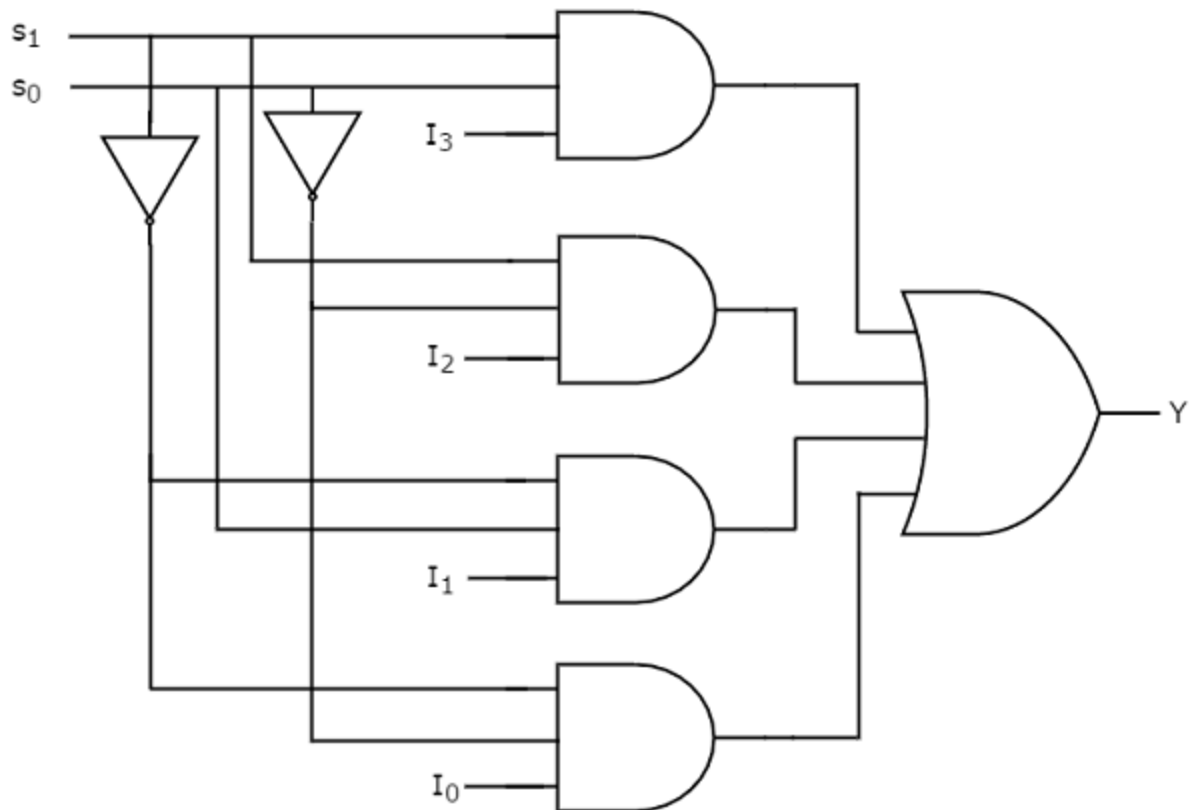

Truth Table

Inputs						Output
S1	S0	I3	I2	I1	I0	Y
0	0	x	x	x	1	1
0	1	x	x	1	x	1
1	0	x	1	x	x	1
1	1	1	x	x	x	1

Code

Implementation

```
architecture Behavioral of mux4x1 is
    signal t1, t2, t3, t4: std_logic;
begin
    t1 <= (X(0) and (not s(0)) and (not s(1)));
    t2 <= (X(1) and s(0) and (not s(1)));
    t3 <= (X(2) and (not s(0)) and s(1));
    t4 <= (X(3) and s(0) and s(1));

    y <= (t1 or t2 or t3 or t4);
end Behavioral;
```

Test Bench

```
ARCHITECTURE behavior OF mux4x1_test_bench IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT mux4x1
    PORT(
        X : IN  std_logic_vector(3 downto 0);
        s : IN  std_logic_vector(1 downto 0);
        Y : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal X : std_logic_vector(3 downto 0) := (others => '0');
    signal s : std_logic_vector(1 downto 0) := (others => '0');

    --Outputs
    signal Y : std_logic;
```

```

BEGIN
  -- Instantiate the Unit Under Test (UUT)
  uut: mux4x1 PORT MAP (
    X => X,
    S => s,
    Y => Y
  );

  stim_proc: process
    variable s_bin: std_logic_vector(1 downto 0);
    variable binary: std_logic_vector(3 downto 0);
  begin
    for i in 0 to 3 loop
      proc_s: dec_to_bin_proc(i, 2, s_bin);
      s <= s_bin;
      for k in 0 to 15 loop
        proc: dec_to_bin_proc(k, 4, binary);
        X <= binary;
        wait for 1ps;
      end loop;
    end loop;
  end process;
END;


```

Timing Diagram




8x1 Multiplexer

Block Diagram

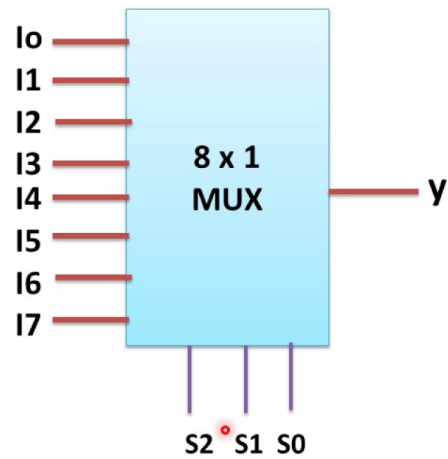

Circuit Diagram

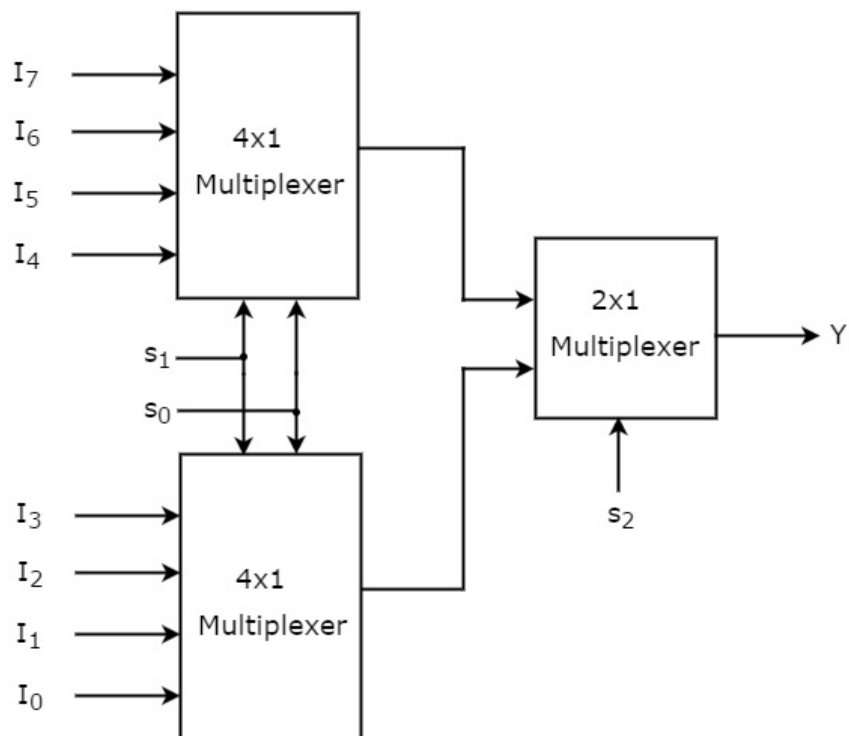

Truth Table

Inputs			Output
S2	S1	S0	Y
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7

Code

Implementation

```

architecture Behavioral of mux8x1 is

    COMPONENT mux4x1
        PORT (
            X : IN  std_logic_vector(3 downto 0);
            s : IN  std_logic_vector(1 downto 0);
            Y : OUT std_logic
        );
    END COMPONENT;

    COMPONENT mux2x1
        PORT (
            X : IN  std_logic_vector(1 downto 0);
            s : IN  std_logic;
            Y : OUT std_logic
        );
    END COMPONENT;

    signal t: std_logic_vector(1 downto 0);
begin
    c1: mux4x1 port map(X(7 downto 4), s(1 downto 0), t(0));
    c2: mux4x1 port map(X(3 downto 0), s(1 downto 0), t(1));
    C3: mux2x1 port map(t, s(2), Y);

end Behavioral;

```

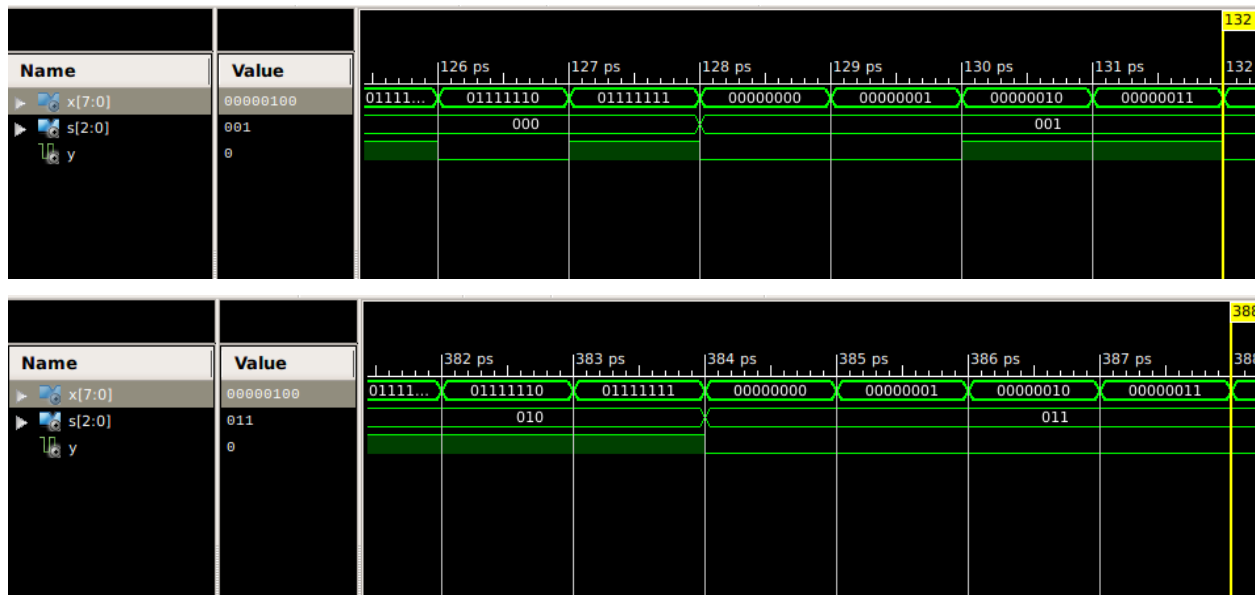

Test Bench

```
ARCHITECTURE behavior OF mux8x1_test_bench IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT mux8x1
    PORT (
        X : IN  std_logic_vector(7 downto 0);
        s : IN  std_logic_vector(2 downto 0);
        Y : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal X : std_logic_vector(7 downto 0) := (others => '0');
    signal s : std_logic_vector(2 downto 0) := (others => '0');
    --Outputs
    signal Y : std_logic;
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: mux8x1 PORT MAP (
        X => X,
        s => s,
        Y => Y
    );


    -- Stimulus process
    stim_proc: process
        variable s_bin: std_logic_vector(2 downto 0);
        variable binary: std_logic_vector(7 downto 0);
    begin
        for i in 0 to 7 loop
            proc_s: dec_to_bin_proc(i, 3, s_bin);
            s <= s_bin;
            for k in 0 to 127 loop
                proc: dec_to_bin_proc(k, 8, binary);
                X <= binary;
                wait for 1ps;
            end loop;
        end loop;
    end process;
END;
```

Timing Diagram



16x1 Multiplexer

Block Diagram

 


Truth Table

Inputs				Output
S3	S2	S1	S0	Y
0	0	0	0	I0
0	0	0	1	I1
0	0	1	0	I2
0	0	1	1	I3
0	1	0	0	I4
0	1	0	1	I5
0	1	1	0	I6
0	1	1	1	I7
1	0	0	0	I8
1	0	0	1	I9
1	0	1	0	I10
1	0	1	1	I11
1	1	0	0	I12
1	1	0	1	I13
1	1	1	0	I14
1	1	1	1	I15

Using 8x1 and 2x1 Multiplexers

Circuit Diagram

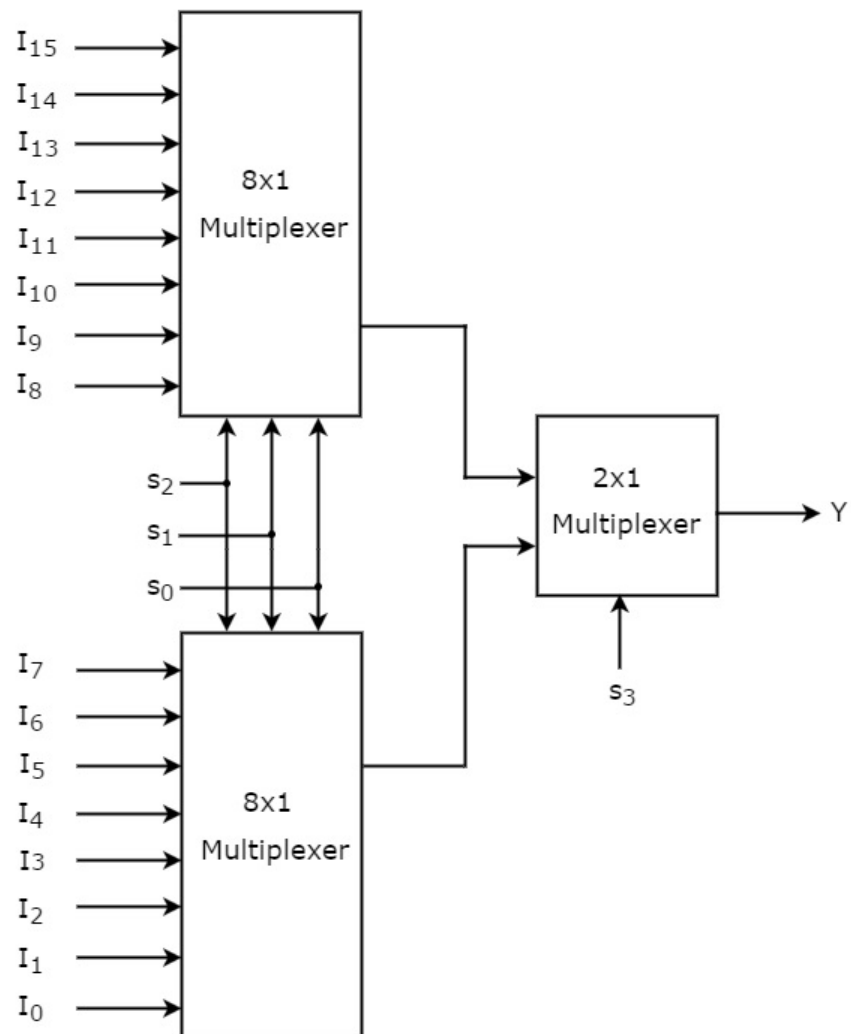

Code

```
entity mux16x1 is
    Port ( X : in  STD_LOGIC_VECTOR (15 downto 0);
          s : in  STD_LOGIC_VECTOR (3 downto 0);
          Y : out  STD_LOGIC);
end mux16x1;

architecture Behavioral of mux16x1 is
    COMPONENT mux8x1
        PORT (
            X : IN   std_logic_vector(7 downto 0);
            s : IN   std_logic_vector(2 downto 0);
            Y : OUT  std_logic
        );
    END COMPONENT;

    COMPONENT mux2x1
        PORT (
            X : IN   std_logic_vector(1 downto 0);
            s : IN   std_logic;
            Y : OUT  std_logic
        );
    END COMPONENT;


    signal t: std_logic_vector(1 downto 0);
begin

    c1: mux8x1 port map(X(15 downto 8), s(2 downto 0), t(0));
    c2: mux8x1 port map(X(7 downto 0), s(2 downto 0), t(1));
    c3: mux2x1 port map(t, s(3), Y);

end Behavioral;
```

Using 4x1 Multiplexers

Circuit Diagram

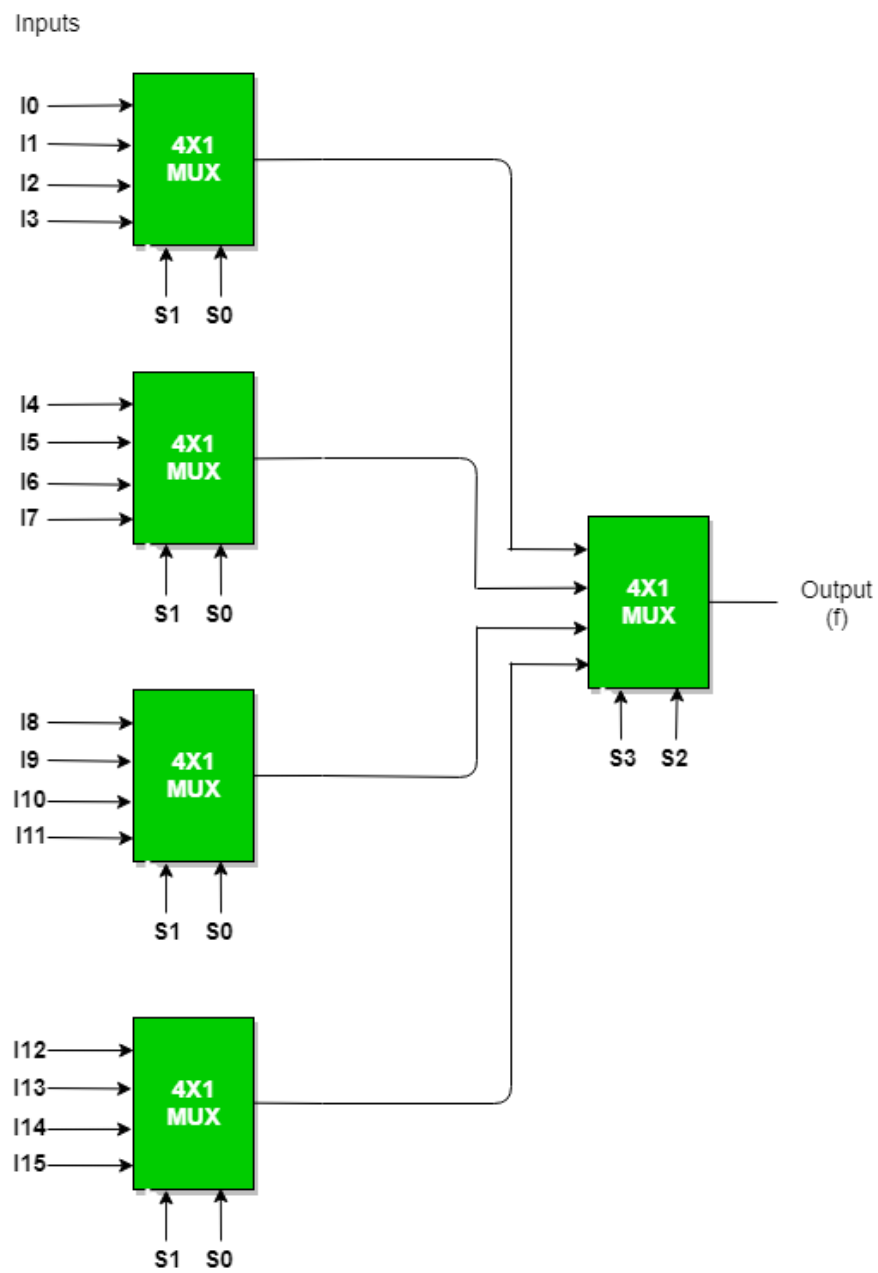

Code

```
architecture Behavioral of mux16x1b is
  COMPONENT mux4x1
    PORT(
      X : IN  std_logic_vector(3 downto 0);
      s : IN  std_logic_vector(1 downto 0);
      Y : OUT std_logic
    );
  END COMPONENT;

  signal t: std_logic_vector(3 downto 0);
begin
  c1: mux4x1 port map(X(15 downto 12), s(1 downto 0), t(3));
  c2: mux4x1 port map(X(11 downto 8), s(1 downto 0), t(2));
  c3: mux4x1 port map(X(7 downto 4), s(1 downto 0), t(1));
  c4: mux4x1 port map(X(3 downto 0), s(1 downto 0), t(0));
  c5: mux4x1 port map(t, s(3 downto 2), Y);
end Behavioral;
```

Test Bench

```
ARCHITECTURE behavior OF mux16x1_test_bench IS
  -- Component Declaration for the Unit Under Test (UUT)
  COMPONENT mux16x1b
    PORT(
      X : IN  std_logic_vector(15 downto 0);
      s : IN  std_logic_vector(3 downto 0);
      Y : OUT std_logic
    );
  END COMPONENT;

  --Inputs
  signal X : std_logic_vector(15 downto 0) := (others => '0');
  signal s : std_logic_vector(3 downto 0) := (others => '0');

  --Outputs
  signal Y : std_logic;
BEGIN
  -- Instantiate the Unit Under Test (UUT)
  uut: mux16x1b PORT MAP (
    X => X,
    s => s,
    Y => Y
  );
```

```

-- Stimulus process
stim_proc: process
  variable s_bin: std_logic_vector(3 downto 0);
  variable binary: std_logic_vector(15 downto 0);
begin
  for i in 0 to 15 loop
    proc_s: dec_to_bin_proc(i, 4, s_bin);
    s <= s_bin;
    for k in 0 to 256 loop
      proc: dec_to_bin_proc(k, 16, binary);
      X <= binary;
      wait for 1ps;
    end loop;
  end loop;

end process;

END;

```

Timing Diagram

