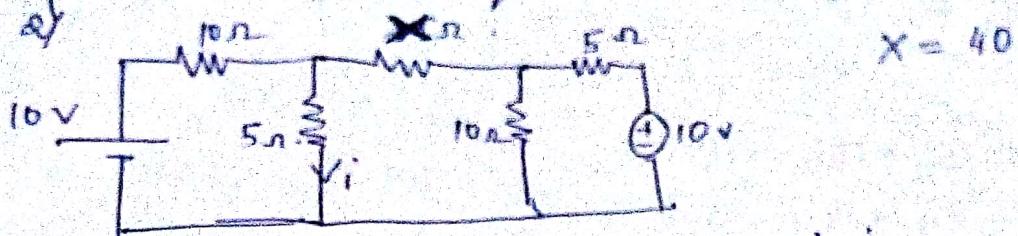


Assignments

1) Derive the vector form of ohm's law!


2)




Find the value of i .

3) Derive the inter relationship ~~between~~ between star & Delta

4).

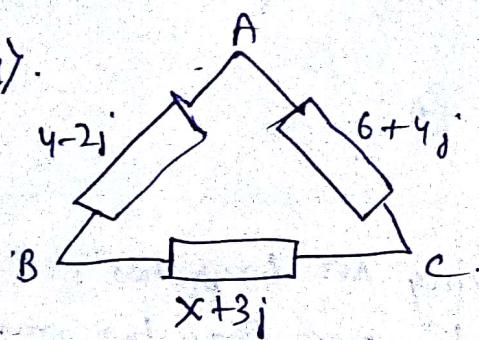

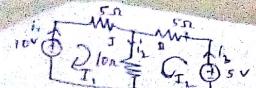5) Prove the maximum power transfer for a.c circuit.



Branch currents (i_1, i_2)
Loop currents

$$10 = 5i_1 + 10i_2 \quad \text{---(1)}$$

$$5 = 5i_2 + 10i_1 \quad \text{---(2)}$$

By
KVL


$$3i_1 + 2i_2 = 2$$

$$2i_1 + 3i_2 = 1$$

$$\therefore i_1 = \frac{4}{5} \text{ A} \quad i_2 = -\frac{1}{5} \text{ A}$$

$$\therefore i_1 = \frac{4}{5} \text{ A} \quad i_2 = -\frac{1}{5} \text{ A} \quad i_3 = \frac{2}{5} \text{ A}$$

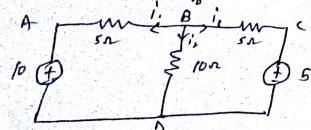By KCL, 0 Junction is a point having two branches.
Nodes is a point having more than two branches.



At B,


$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{v_B - 10}{5} + \frac{v_B - 0}{10} + \frac{v_B - 5}{5} = 0$$

$$\Rightarrow \frac{4v_B}{10} + \frac{v_B}{10} = 3$$

$$\Rightarrow v_B = 6 \text{ V}$$
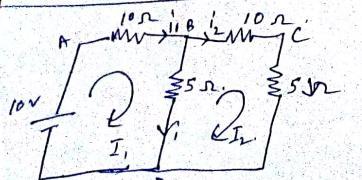
$$i_1 = -\frac{4}{5} \quad i_2 = \frac{3}{5} \quad i_3 = \frac{1}{5}$$



$$10 = 10i_1 + 5i$$

$$10i_2 + 5i_3 - 5i = 0$$

$$i_1 = i + i_2$$

$$\Rightarrow 10 = 10i_1 + 10i_2 + 5i$$

$$\text{---(3)} \quad 15i_2 - 5i = 0$$

$$\Rightarrow i = 3i_2$$

$$\begin{aligned} & \Rightarrow 15i + 10i_2 = 10 \\ & \Rightarrow 15i + \frac{10}{3}i = 10 \\ & \Rightarrow \frac{55}{3}i = 10^2 \Rightarrow i = \frac{6}{11} \text{ A} \end{aligned}$$

By KCL,



$$\frac{v_B - 10}{10} + \frac{3v_B}{15} + \frac{v_B}{75} = 0$$

$$\Rightarrow \frac{v_B}{10} + \frac{4v_B}{15} = 1$$


$$\Rightarrow \frac{3v_B + 8v_B}{30} = 1 \Rightarrow v_B = \frac{30}{11} \text{ V}$$

$$\therefore i = \frac{3v_B}{5} = \frac{6}{11} \text{ A}$$
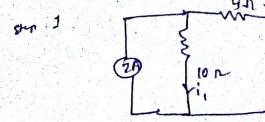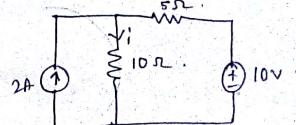
$$\frac{4v_A}{10} + \frac{v_A}{10} = 3 \Rightarrow v_A = 6 \text{ V}$$



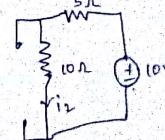
$$\text{Current } i_{10} = \frac{5}{15} \times 2 = \frac{2}{3} \text{ A}$$



$$\text{Current } i_{12} = \frac{10}{15} = \frac{2}{3} \text{ A}$$
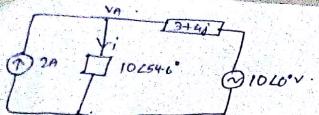
$$\therefore i_1 + i_2 = \frac{4}{3} \text{ A}$$



$$2 = \frac{V_A}{10\angle 54.6^\circ} + \frac{V_A - 10}{3 + 4j}$$

$$2 = \frac{V_A}{5.8 + j8.15} + \frac{V_A - 10}{3 + 4j}$$

$$\Rightarrow 2 = (3+4j)V_A + (-5+8j)(V_A - 10)$$

~~RA RB RC~~

Y-Delta Transform.

RA, RB & RC known.



$$\therefore R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A \times R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_B \times R_C}{R_A + R_B + R_C}$$

Star - Delta




Given R₁, R₂, R₃ known.

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

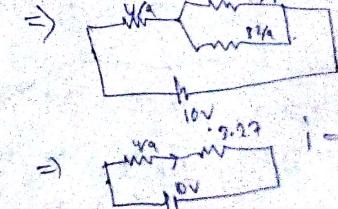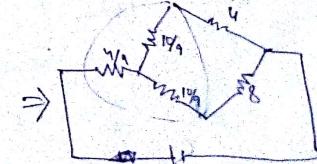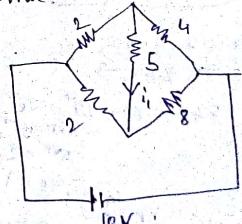Find out the total current in the circuit.



$$i = 2.68A$$

Step 1

$$i_1 = \frac{10\angle 60^\circ}{5-j3} = \frac{10\angle 60^\circ}{5.83 \angle -30.9^\circ} = 1.715 \angle 90.9^\circ.$$

Step 2

$$i_1 = \frac{j3}{5-j3} \times 120^\circ = \frac{3\angle 90^\circ}{5.83 \angle -30.9^\circ} = 0.515 \angle 120.9^\circ.$$

$$\therefore i = (-0.026 + j1.715) + (-0.264 + j0.444) = (-0.290 + j2.157) A. \quad \text{in}$$

$$= 2.176 \angle 97.6^\circ A$$

Thevenin's Theorem:

Any linear active network consisting of dependent & independent sources and linear bilateral network elements can be replaced by an equivalent circuit consisting of a voltage source in series with a resistance, the voltage source being the open circuited voltage across the open circuited load terminals and the resistance being the internal resistance of the source network looking through the open circuited load terminals with all the active sources either replaced by their internal resistances (if any) or short circuited (In case of voltage source) or open circuited (In case of current source).

Applying Thevenin's theorem

$$R_{TH} = 12.5 \Omega.$$

$$V_{TH} = 5V.$$

$$\therefore \text{Current through } 20\Omega = \frac{5}{32.5} = \frac{1}{6.5} = 0.153 A.$$

In I_L is the current flowing through short circuited load terminals

Maximum Power Transfer theorem:

A resistive load connected to a d.c. network receives max power when the load resistance is equal to the internal resistance of source network as seen from the load terminals i.e. Thevenin's Resistance.

For a.c.

An impedance connected to an a.c. network receives max power when the load impedance is equal to the internal conjugate of the internal impedance of source network as seen from the load terminals i.e. Thevenin impedance.

$$P_L = I_L^2 R_L = \left(\frac{V_{TH}}{R_{TH}+R_L}\right)^2 R_L = \left(\frac{V_{TH}}{R_{TH}+R_L}\right)^2 R_L$$

$$\frac{dP_L}{dR_L} = (V_{TH})^2 \left\{ \frac{(R_{TH} + R_L)^2 - 2R_L(R_{TH} + R_L)}{(R_{TH} + R_L)^3} \right\}$$

$$= (V_{TH})^2 \frac{(R_{TH} - R_L)}{(R_{TH} + R_L)^3}$$

For maximum value of P_L , $\frac{dP_L}{dR_L} = 0$

$$\Rightarrow R_{TH} - R_L = 0 \quad \textcircled{1}$$


$$\Rightarrow R_{TH} = R_L$$

$$\text{Maximum Power} = \frac{(V_{TH})^2 R_L}{4R_L^2} = \frac{(V_{TH})^2}{4R_L} = P_{max}$$

Total power dissipated or provided by a source

$$= 2 \times P_{max} = \frac{V_{TH}^2}{2R_L}$$

Super Node Analysis

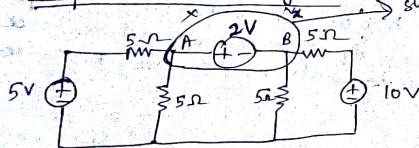

If a voltage source is connected between two nodes, then it is said to be a super node.

Applying KCL at X,

$$\frac{V_A - 5}{5} + \frac{V_A}{5} + \frac{V_B - 10}{5} + \frac{V_B}{5} = 0$$

$$V_A - V_B = 2$$

$$\frac{2V_A}{5} + \frac{2V_B}{5} = 3$$

$$2V_A + 2V_B = 7.5$$


$$V_A - V_B = 2$$

$$2V_A = 9.5 \Rightarrow V_A = 4.75$$

$$V_B = 2.75$$

If a resistance connected in parallel with voltage source then also it will be a super node.

Super Mesh Analysis

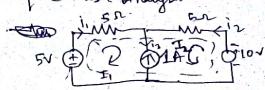

② Current-source being at the junction of two loops



$$5I_2 + 5 = 5I_1 + 10 \quad \textcircled{1}$$

$$I_1 + I_2 = 1 \quad (\text{not KCL})$$


$$I_1 - I_2 = -1$$

$$\frac{2I_1}{I_1} = -2$$

$$I_1 = -1, I_2 = 0$$

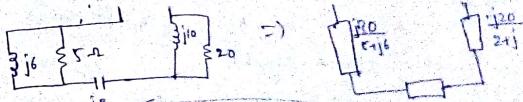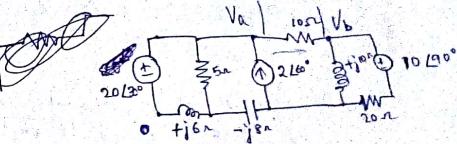
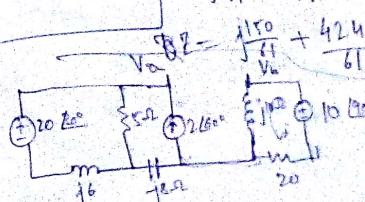
$$Z = 0.261 \angle 11.1^\circ = \frac{j20(s-j6)}{2s+26} = \frac{j20(s-j6)}{61} = j\frac{120}{61} - j\frac{120}{61} + 4$$



$$I = \frac{10}{20+j10} = \frac{10}{26.8} = 0.375$$


$$I = (2-j2) = 0.2 + j0.4$$

$$I = (-4+j2) = V_B - 2.75$$

$$(x+D)^n - u^n = \frac{D}{n} u^{n-1} + u^{\frac{n-1}{2}} u^{n-2} \dots + \frac{D^{n-1}}{n} u^0$$

AC Fundamentals.

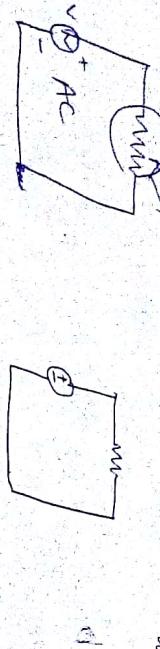RMS value in the current flowing through a circuit which would produce the same amount of heat generated in a resistor, when a.c. signal passes through it in a given amount of time.



Q: Value of a sinusoidal signal transferred over same amount of charge discharged.

In a symmetrical signal, average value is taken for half a cycle. In an asymmetrical, avg. value is taken over full period.

Average value:

$$I_{avg} = \frac{1}{T} \int_0^T i dt$$



$$= \frac{1}{T} \int_0^T I_0 \sin \omega t dt$$

$$= \frac{1}{T} \int_0^T I_0 \sin \omega t dt$$

$$= \frac{I_0}{T} \left[-\frac{1}{\omega} \cos \omega t \right]_0^T$$

$$= \frac{I_0}{T} \left[-\frac{1}{\omega} (\cos 0 - \cos \omega T) \right]$$

$$= \frac{2I_0}{\pi} A$$

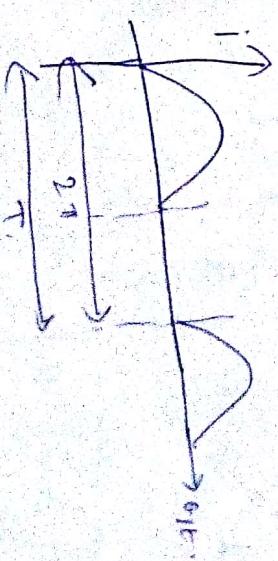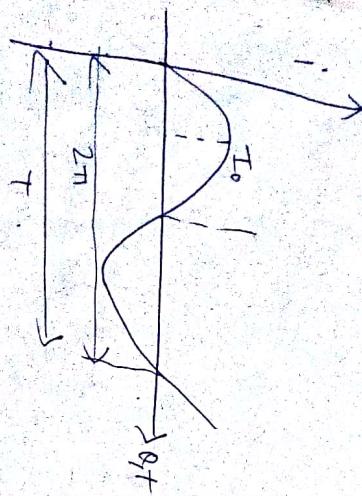

For half wave rectifier,

$$\text{Form factor} = \frac{I_{rms}}{I_{avg}} = \frac{I_0 / \sqrt{2}}{\frac{I_0}{2\pi}} = \frac{\pi}{2\sqrt{2}} = \frac{\pi}{4} \approx 1.11$$

$$\text{Peak factor} = \frac{I_{peak}}{I_{rms}} = \frac{I_0}{I_0 / \sqrt{2}}$$

$$= \sqrt{2} = 1.414$$

$$I_{avg} = \frac{1}{T} \int_0^T i dt$$

$$= \frac{1}{T} \int_0^T I_0 \sin \omega t dt$$

$$= \frac{I_0}{T} \int_0^T \sin \omega t dt$$

$$I_{rms} \text{ for half period} = \frac{1}{\pi} \int_0^{\pi} i^2 d\theta$$

$$= \frac{I_0^2}{\pi} \int_0^{\pi} \sin^2 \theta d\theta = \frac{I_0^2}{\pi} \left[\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right]_0^{\pi}$$

$$= \frac{I_0^2}{2}$$

$$I_{rms} = \sqrt{\frac{I_0^2}{2}} = \frac{I_0}{\sqrt{2}}$$

$$I_{rms}^2 = \frac{I_0^2 \sin^2 \omega t}{T} dt$$

$$= \frac{I_0^2}{T} \int_0^T \left(\frac{1-\cos 2\omega t}{2} \right) dt$$

$$= \frac{I_0^2}{T} \left[\frac{t}{2} - \frac{\sin 2\omega t}{2\omega} \right]_0^T$$


$$= \frac{I_0^2}{T} \left[\frac{T}{2} \right] = \frac{I_0^2}{2}$$

$$\begin{aligned} I_{r.m.s}^2 &= \frac{1}{2\pi} \int_0^\pi i^2 d\theta + \frac{1}{2\pi} \int_\pi^{2\pi} i^2 d\theta \\ &= \frac{1}{2\pi} \int_0^\pi i^2 d\theta + 0 \\ &= \frac{I_0^2}{2\pi} \int_0^\pi \sin^2 \theta d\theta = \frac{I_0^2}{2\pi} \left[\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right]_0^\pi \\ &= \frac{I_0^2}{4} \end{aligned}$$

$$\therefore I_{r.m.s.} = \frac{I_0}{2}$$

$$\text{Form factor} = \frac{I_0/2}{I_0/\pi} = \sqrt{2} = 1.57$$

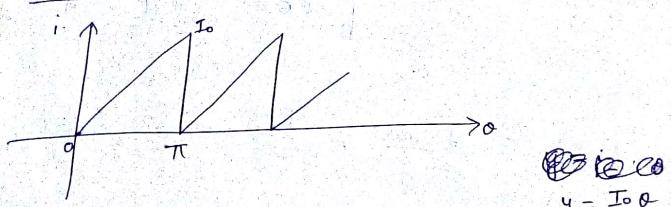
$$\text{Peak factor} = \frac{I_0}{I_0/2} = 2.$$



$$I_{avg} = \frac{I_0 \pi}{2\pi} = \frac{I_0}{2}$$

$$\begin{aligned} I_{r.m.s.} \frac{1}{2\pi} \int_0^{2\pi} i^2 d\theta &= \frac{1}{2\pi} \int_0^\pi i^2 d\theta + \int_\pi^{2\pi} i^2 d\theta \\ &= 2 \int_0^\pi \frac{I_0^2}{\pi^2} \theta^2 d\theta = \frac{I_0^2}{\pi^3} \int_0^\pi \theta^2 d\theta \\ &= \frac{I_0^2}{\pi^3} \left[\frac{\theta^3}{3} \right]_0^\pi \end{aligned}$$
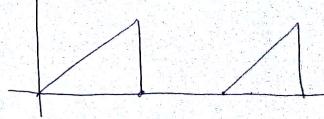
$$\begin{aligned} \text{Form factor} &= \frac{I_0/\sqrt{3}}{I_0/2} = \frac{2}{\sqrt{3}} = 1.154 \\ \text{Peak} &= \frac{I_0}{I_0/2} = \sqrt{3} = 1.732 \end{aligned}$$




$$I_{avg} = \frac{I_0 \pi}{2\pi} = \frac{I_0}{2}$$

$$I_{r.m.s.}^2 = \frac{1}{2\pi} \int_0^\pi \frac{I_0^2}{\pi^2} \theta^2 d\theta = \frac{I_0^2}{\pi^3} \left[\frac{\theta^3}{3} \right]_0^\pi = \frac{I_0^2}{6}$$

$$\therefore I_{r.m.s.} = \frac{I_0}{\sqrt{6}}$$
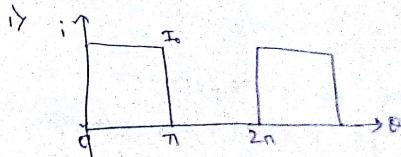
$$\begin{aligned} \text{FF} &= \frac{4}{\sqrt{6}} & P.F. &= \sqrt{6} \\ &= 1.6329 & &= 2.45 \end{aligned}$$




$$I_{avg} = \frac{I_0 \pi}{2\pi} = \frac{I_0}{2}$$

$$I_{r.m.s.}^2 = \frac{1}{2\pi} \int_0^\pi I_0^2 d\theta = \frac{I_0^2}{2}$$

$$\therefore I_{r.m.s.} = I_0/\sqrt{2}$$
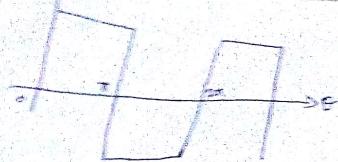
$$\begin{aligned} \text{FF} &= \sqrt{2}. & P.F. &= \sqrt{2} = 1.414 \\ & & &= 1.414 \end{aligned}$$



$$I_{\text{avg}} = \frac{I_0 \pi}{2\pi} = I_0$$


$$I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I^2 d\theta} = \frac{I_0}{\pi} \left[\theta \right]_0^{2\pi} = I_0$$

$$\therefore I_{\text{rms}} = I_0$$

$$\therefore P \cdot F = 1 \quad , \quad FF = 1.$$

$F \cdot F$ is always greater than 1
But for symmetrical square it has a value $\frac{m}{l}$


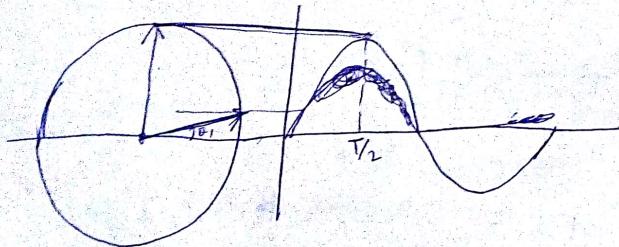
Only sinusoidal quantities can be represented as a phasor diagram.
And magnitude of the phasor is the r.m.s value of the quantity.




In a resistive circuit, current is in same phase with voltage.

For induction circuit
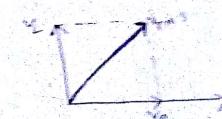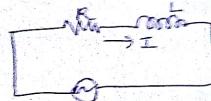
$$V = V_{\text{sin} \omega t} \quad I_L = \frac{V}{jX_L} = \frac{V_{\text{sin} \omega t}}{jX_L} = \frac{V_0 \sin(\omega t - 90^\circ)}{X_L}$$



For RLC,

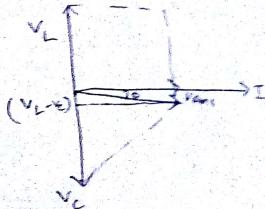

Final angle or phase between V_{rms} & I_{rms}
= power factor angle

$$\text{Apparent power} = V_{\text{rms}} I_{\text{rms}} = \sqrt{V^2_{\text{rms}} + I^2_{\text{rms}}}$$


Watt is the unit of active power
power available for work

$$\text{Active power} = V_{\text{rms}} I_{\text{rms}} \cos \theta \rightarrow \text{Watt}$$


$$\text{Reactive power} = V_{\text{rms}} I_{\text{rms}} \sin \theta \quad (\text{Not available for work})$$

$$\text{Power factor} = \frac{\text{Active power}}{\text{Apparent power}} = \frac{P}{S} = \frac{P}{\sqrt{P^2 + Q^2}}$$

VAR
volt-ampere reactive

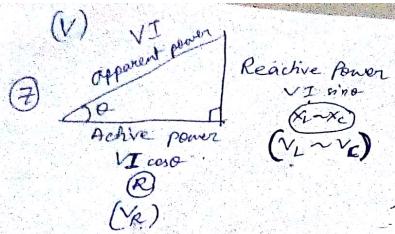

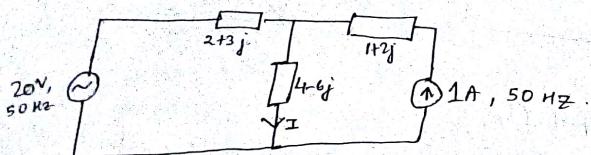(J) — \emptyset Voltage
 ○ — \emptyset Resistance
 - Power



$$i_1 = \frac{20}{(2+3j) + (4-6j)} = \frac{20}{6-3j} = \frac{20(6+3j)}{36+9} = \frac{60(2+j)}{45} = \frac{8+4j}{3}$$


$$i_2 = 1 \quad \therefore I = \frac{11}{3} + \frac{4}{3}j = 3.67 + 1.33j \quad \text{A}$$

$$\frac{(2+3j)(4-6j)}{6-3j} + 1+2j \quad \checkmark$$

$$\frac{26}{6-3j} + 1+2j = \frac{26 + (1+2j)(6-3j)}{6-3j} = \frac{26 + 12 + 9j}{6-3j} = \frac{38+9j}{6-3j}$$

$$\frac{2+3j}{6-3j} = \frac{(2+3j)(6+3j)}{6-3j} = \frac{3+24j}{6-3j}$$
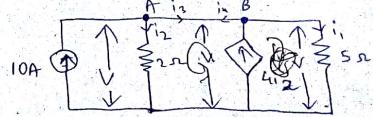
$$I = \left(\frac{8}{3} + \frac{3}{9}\right) + j\left(\frac{24}{6} + \frac{4}{3}\right) = 2.733 + 1.867 = 3.334 \text{ A}$$



$$10 + 3i_2 = i_1$$


$$\frac{V}{5} = i_1$$

$$\frac{V}{2} = i_2$$

$$10 = i_3 + i_2 \\ = -(4i_2 - i_1) + i_2 \\ 10 + 3i_2 = i_1$$

$$10 + \frac{3V}{2} = \frac{V}{5} \\ \Rightarrow 10 = \frac{-13V}{10} \Rightarrow V = -\frac{100}{13}$$

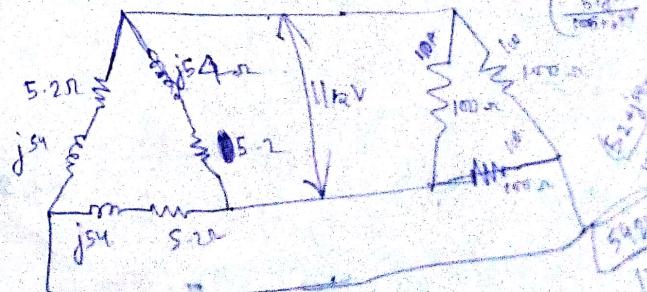
$$\therefore i_1 = -\frac{100}{65} = -\frac{20}{13} \quad i_2 = -\frac{100}{26}$$



Transformer:


Static electromagnetic device

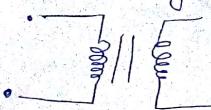Flux energy is transferred from one part of circuit to another which are electrically isolated and magnetically coupled.




Types of transformer .

core type

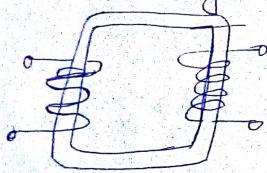

shell type .

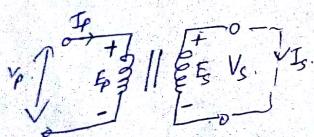

Flux generated by V_p

$$\phi = \phi_m \sin \omega t$$

$$e = -N \frac{d\phi}{dt} = -N \phi_m \omega \cos \omega t \\ = e_0 \cos \omega t, e_0 = -N \phi_m \omega$$

$$|E_{0-m.s}| = \frac{1}{\sqrt{2}} N \phi_m \omega = \sqrt{2} \pi f N \phi_m$$

$$E_{0-m.s} = 4.44 f N \phi_m$$

$$= 4.44 f N B_m A$$

$$E_p = 4.44 f N_p B_m A$$

$$E_s = 4.44 f N_s B_m A$$

$$\frac{E_p}{E_s} = \frac{N_p}{N_s} = \text{turns ratio}$$

$$\frac{E_p I_p}{E_s I_s} \underset{\text{constant}}{\equiv} \Rightarrow \frac{N_p I_p}{N_s I_s} = \text{constant}$$

$$\frac{I_p}{I_s} = \frac{N_s}{N_p}$$

Amperes turns of primary
= amperes turns of secondary

$$\text{Power} = \frac{I_p^2 Z_p}{I_s^2 Z_s} = \text{constant}$$

$$\Rightarrow \frac{N_s^2 Z_p}{N_p^2 Z_s} = \text{const} \Rightarrow \frac{Z_p}{Z_s} = \frac{N_p^2}{N_s^2}$$

A 1 kVA 200V / 300V single phase transformer has 200 turns in the secondary. Find out the turns ratio, no. of turns in primary, current flowing in primary and the ratio of primary & secondary impedance.



$$\frac{200}{300} = \frac{N_p}{200} \Rightarrow N_p = \frac{400}{3}$$

$$\text{turns ratio} = \frac{2}{3}$$

$$\text{Apparent power} = 1000 \text{ VA}$$

$$1000 = 200 \times I_p \Rightarrow I_p = 5$$
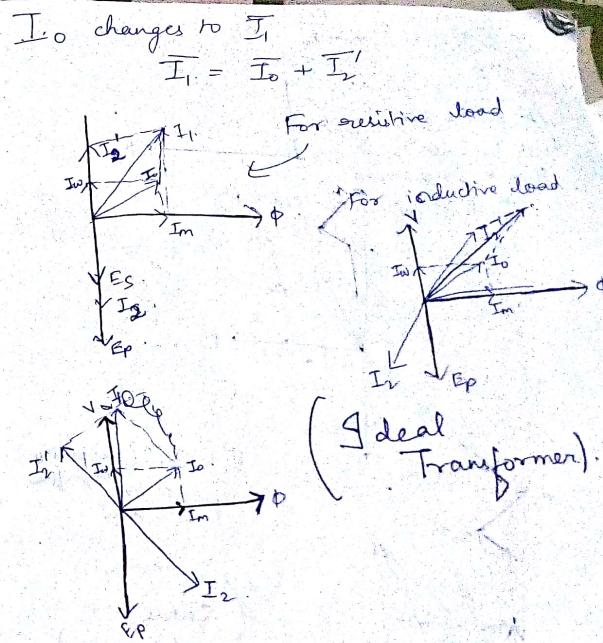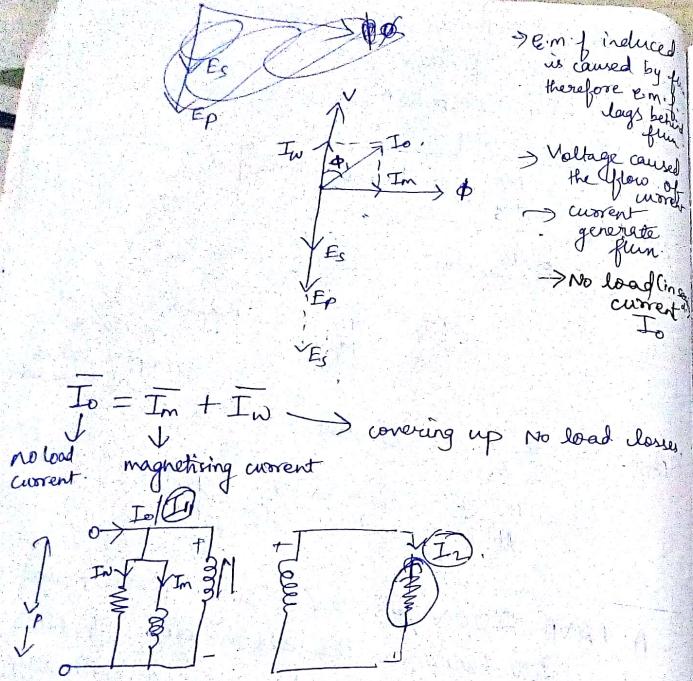
$$\text{Ratio of primary to secondary} = \frac{I_p}{I_s}$$






$$I_m = I_o \sin \phi, \quad I_w = I_o \cos \phi.$$

Singlephase : I_m is 5% of I_o (Experimental)

When load is connected to secondary, current will flow \rightarrow flux is created \rightarrow to negate this flux more flux is generated in primary which makes the transformer draw more current from primary.


For Practical transformer,

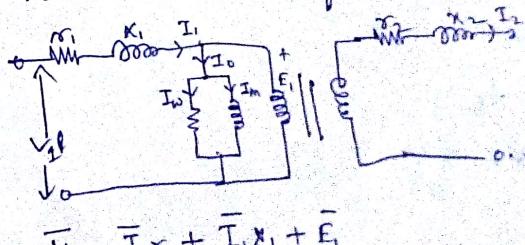

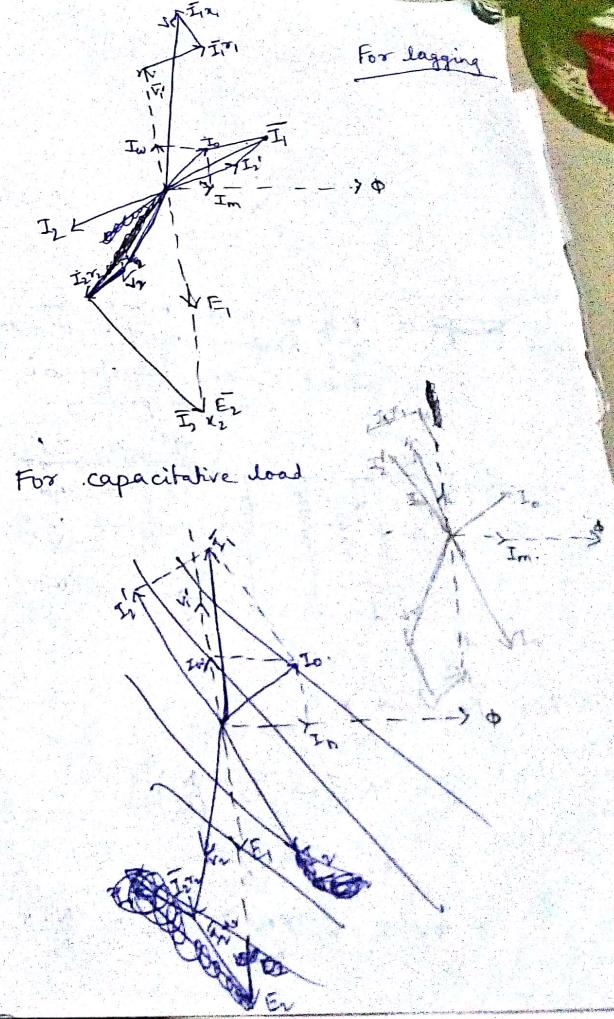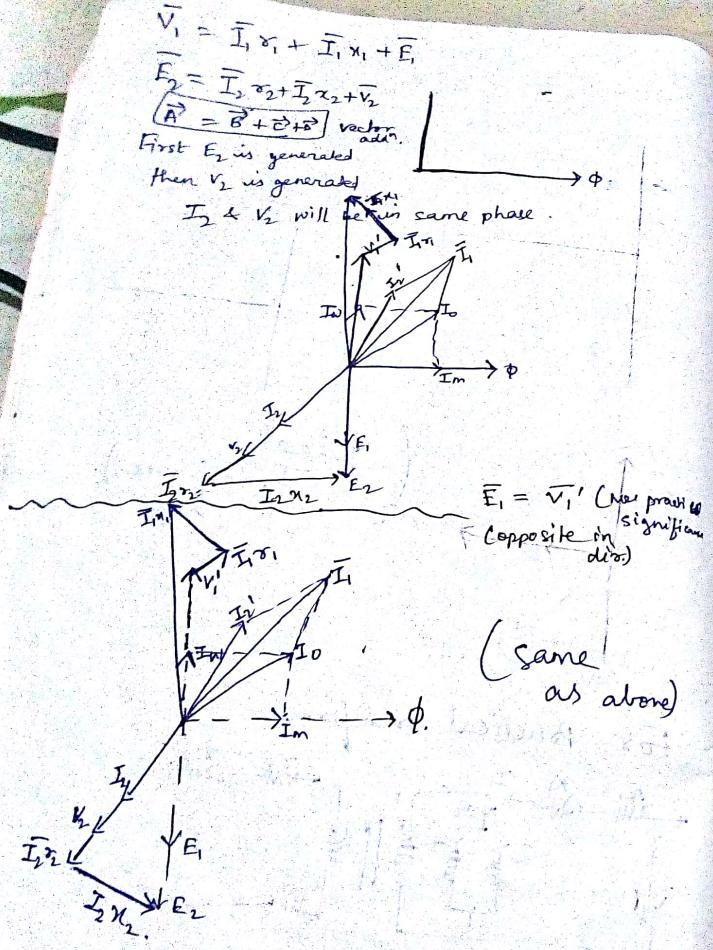

Transformer

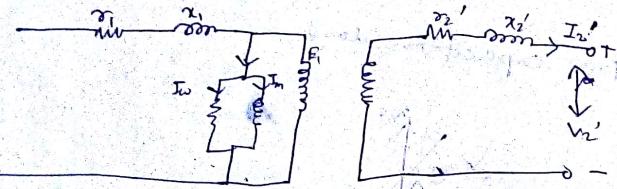- If we convert E_1 to E_2 , we say transformer is ref. to secondary.
- If we convert E_2 to E_1 , transformer is ref. to primary.



For N_2 turns,


$$N_2 \rightarrow x_2$$

$$N_1' \rightarrow x_2 \times \left(\frac{N_1}{N_2}\right)^2$$


$$x_2' = x_2 \left(\frac{N_1}{N_2}\right)^2$$

$$x_2' = x_2 \left(\frac{N_1}{N_2}\right)^2 \quad I_2' = \frac{N_2}{N_1} I_2$$

Approx. equivalent circuit.

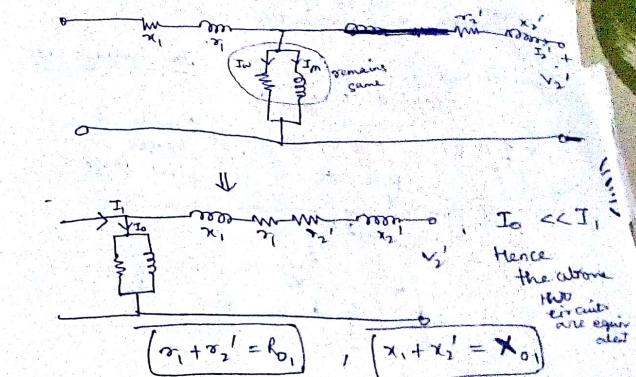

refer to secondary.

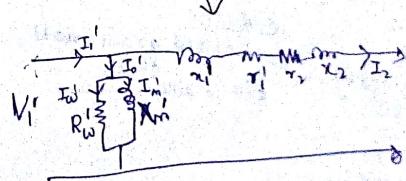

$$\frac{E_1'}{E_1} = \frac{N_2}{N_1}$$

$$E_1' = \left(\frac{N_2}{N_1}\right) E_1$$

$$x_1' = \left(\frac{N_2}{N_1}\right)^2 x_1$$

$$I_1' = \frac{N_1}{N_2} I_1$$

$$I_2' = \frac{N_2}{N_1} I_2$$

$$R_{02}' = \left(\frac{N_2}{N_1}\right)^2 R_{02}$$


$$X_{02}' = x_1' + x_2'$$

Short circuit test & open circuit test is used to obtain the parameters.

Open circuit test is applied to low-voltage side
(Rated voltage is applied)

• 1 KVA 100V/400V

Wattmeter.

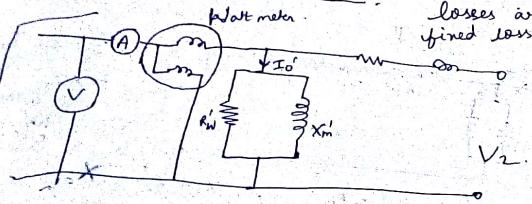

No load losses Hysteresis loss

Hysteresis loss can be reduced by using CRGOS

CRGOS
cold rolled grain oriented steel with a little bit silicon

Eddy currents can be reduced by lamination

Results of OC Test

• Rated voltage $\approx 100V$, Current $= 1A$, 50 W

$$\cos \phi_0 = \frac{P}{V I_0} = 0.5$$

$$\sin \phi_0 = 0.867$$


$$I_m = 0.867 A$$

$$I_w = 0.5 A$$

$$X_m = \frac{100}{0.867} = 115.34 \Omega$$

$$R_w = \frac{100}{0.5} = 200 \Omega$$

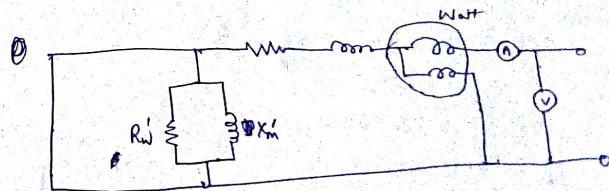② short circuit test is preferably applied on ~~the~~ high voltage side.
Low voltage side is short circuited.
Rated current is applied.



Reading : 40V, 2.5A, 80W

↓
Ohmic loss.

(Full load loss)

$$I^2 R_{02} = 80$$

$$\Rightarrow R_{02} = \frac{80}{6.25} \quad I = 2.5$$

$$= 12.8$$

$$Z_{02} = \frac{40}{2.5} = 16 \Omega \quad K_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = 9.6$$

$$R_{01} = 12.8 \times \left(\frac{100}{400}\right)^2 \Omega$$

$$X_{01} = 9.6 \times \left(\frac{100}{400}\right)^2$$

5 kVA, 500V/200V

OC Test: 200V, 1.5 A, 80 W

SC Test: 50V, 10A, 200W

Parameters ref. to primary & secondary.

$$\cos \phi_0 = \frac{W_0}{VI_0} = \frac{80}{300} = \frac{4}{15}$$

$$\sin \phi_0 = 0.963$$

$$I_m = 1.444 \text{ A}$$

$$I_w = 0.4 \text{ A}$$

$$R_{01} = \frac{200}{0.4} = 500 \Omega$$

$$X_M = 138.456 \Omega$$

Ohmic loss = 200

$$\Rightarrow 10^2 \times R_{0f} = 200$$

$$\Rightarrow R_{0f} = 2 \Omega$$

$$Z_{0f} = 5 \Omega \quad X_{0f} = \sqrt{25 - 4} = 4.88 \Omega$$

~~$$R'_{01} = (2.5)^2 \times 2 = 12.5$$~~

$$X'_{01} = (2.5)^2 \times 4 = 25$$

Referred to low voltage

$$R_{02} = R_{01} \times \left(\frac{1}{2}\right)^2 = 0.32$$

$$X_{02} = X_{01} \times \left(\frac{1}{2}\right)^2 = 0.733$$

R_W, X_M remains same

Referred to high voltage.

$$\bullet R'_W = R_W \times \left(\frac{500}{100}\right)^2$$

$$\bullet X'_M = X_M \times \left(\frac{500}{100}\right)^2$$

10 kVA, 1000V / 500V

OC test $\rightarrow 500V, 2A, 100W$ (W.s + loss/second)

SC test $\rightarrow 50V, 10A, 300W$

$$\cos \phi_0 = \frac{W_0}{VI_0} = \frac{100}{1000} = 0.1$$

$$\sin \phi_0 = 0.995$$

$$I_m = I_0 \times 0.1 = 0.1 \text{ A}$$

$$I_w = I_0 \times 0.995 = 0.995 \text{ A}$$

$$R_W = 251.3 \Omega$$

$$\bullet X_M = 2500 \Omega$$

$$\textcircled{1} \quad Z_{01} = 5 \Omega$$

$$\therefore X_{01} = 4 \Omega$$

Referred to low voltage transformer side,

$$\textcircled{2} \quad R_{02}' = R_{01} \left(\frac{1}{n} \right) = \frac{1}{4} = 0.25 \Omega$$

$$X_{02}' = X_{01} \left(\frac{1}{n} \right) = 1 \Omega$$

Referred to high voltage side,
 R_W & X_M are constant.


$$R_W' = R_W \times 4 = 100 \Omega$$

$$X_M' = X_M \times 4 = 10000 \Omega$$

Voltage Regulation


Fractional change in voltage

Efficiency

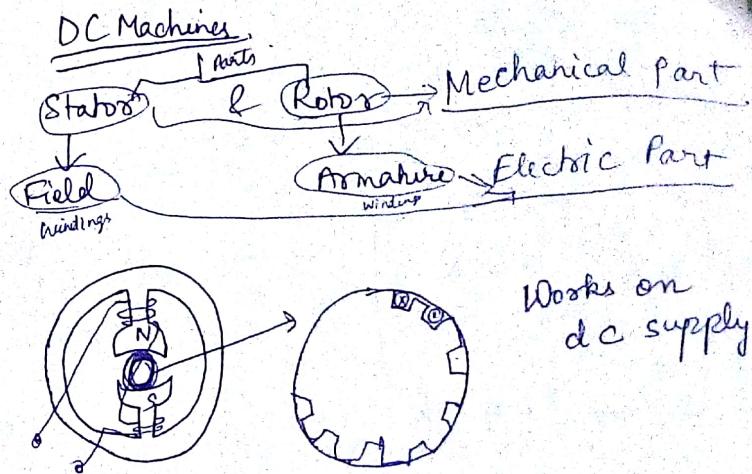


Symbol for dc machines.

Excitations.

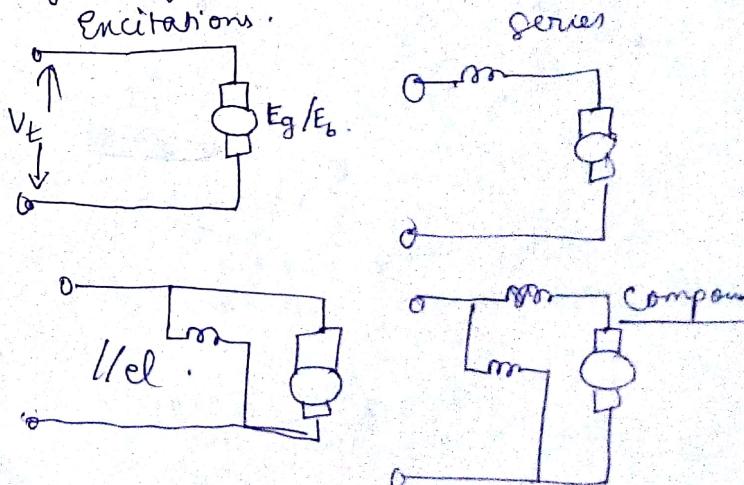

(Brush & Commutator Assembly) in a d.c. machine

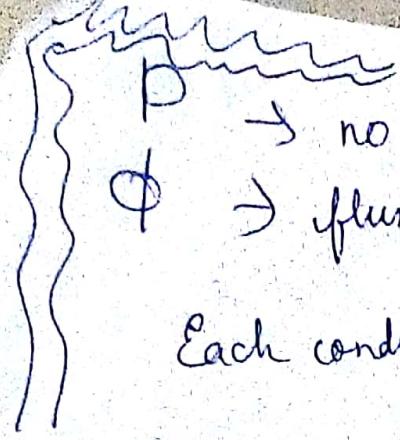
 P → no. of poles
 φ → flux due to each pole.
 Each conductor cuts $P\phi$ flux in one complete rotation.

⇒ Conductors are connected in A parallel paths connected in series.

$$\begin{aligned}
 e &= \frac{d\phi}{dt} = \frac{P\phi}{60N} \\
 &= \frac{P\phi N}{60} \\
 \text{induced in one conductor}
 \end{aligned}$$


N rpm is the speed

$$\begin{aligned}
 \text{e.m.f for one parallel path} &= \frac{P\phi N Z}{60 \times A} \\
 &= \frac{P\phi N Z}{60 \times A}
 \end{aligned}$$



Known as generated e.m.f
in case of generator

Back e.m.f in case of motor



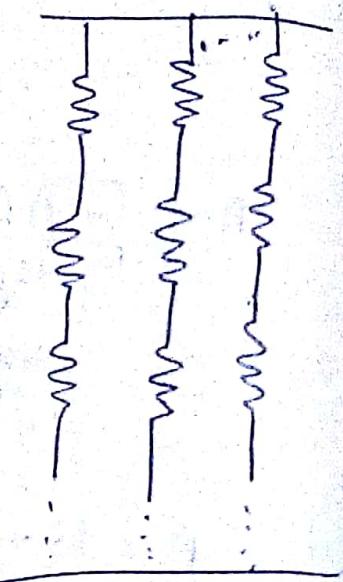


Types of Armature winding connection:

1) Wave connection → $A = 2 \times f$

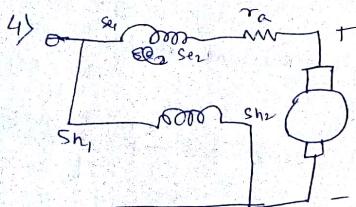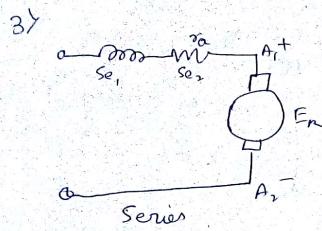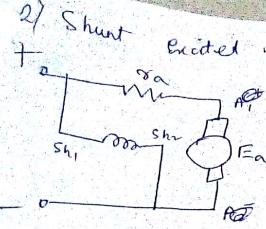
2) Lap " → $A = P \times f$.

simple, Double, Triple
 $f=1$ $f=2$ $f=3$.



V1.
Compound-

As a generator

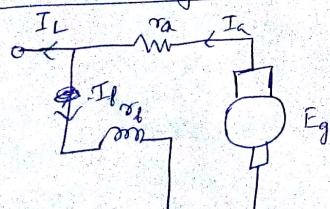

$$I_a = I_L + I_f$$

$$I_b = V_T / r_b$$

$$E_g = V_T + I_a \cdot r_a$$

As a motor
direction of I_L & I_a reverses

$$I_L = I_a + I_f$$

$$\sqrt{t} = E_b + I_a \cdot r_a$$

$$E_g = \frac{P \Phi_g N g Z}{60 A}$$

$$E_b = \frac{P \Phi_m N m Z}{60 A}$$

$$\boxed{E_g/E_b = \frac{\Phi_g N g}{\Phi_m N m}}$$

In a dc shunt M/C, field flux remains constant

A 300 V d.c. ^{shunt} M/C, takes a load current of 5A, the field resistance is 20Ω, armature resistance is 1Ω. Find out the ratio of the speed of the machine as a generator & motor

As a generator

$$I_b = \frac{300}{200} = 1.5 A, I_L = 5 A$$

$$\therefore I_a = 6.5 A$$

$$E_g = 300 + 6.5 \times 1 = 306.5 V$$

As a motor,

$$I_L = I_a + I_f$$

$$\Rightarrow 5 = I_a + 1.5 \Rightarrow I_a = 3.5$$

$$\therefore E_b = 300 - 3.5 \times 1 = 296.5 V$$

$$\therefore \frac{N_g}{N_m} = \frac{E_g}{E_b} = \frac{306.5}{296.5} = \frac{613}{595} = 1.033$$

Armature Reaction

Reaction to armature current
 → generation of armature flux
 → leading to reduction of main field
 → distortion of flux wave


Solution to detrimental effects of Armature react.:

(1) Compensating Windings
 It counteracts the flux generated by armature.


Interpoles

Characteristics of D.C. generators:

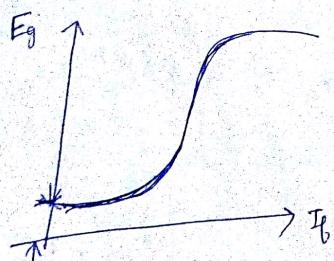
- No load characteristics (E_g vs I_f)
- Load " (V_t vs I_f)
- External " (V_t vs I_L)
- Armature " (I_f vs I_a)



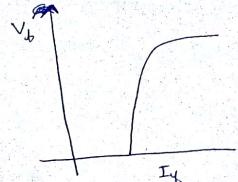
No load characteristic
 for ALL the four diff excitation modes.



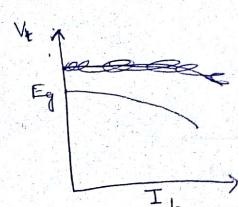Load characteristic
 for Separately excited L series & shunt




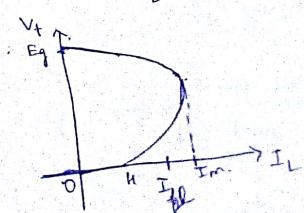External characteristics
 for separately excited



for shunt Φ .

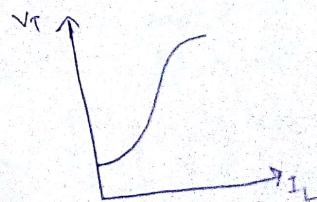I_{m} = Max load curr.
 I_{fL} = Full load curr.
 I_R = Current due to residual flux




For series

For compound.



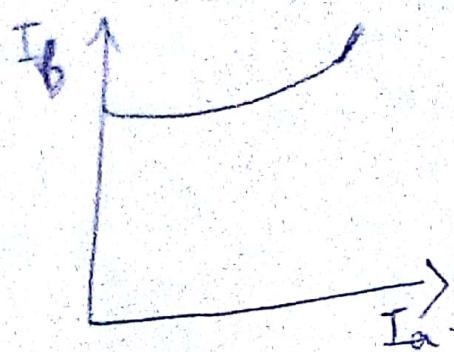Armature characteristic for separately excited D.C. generator



Torque equation of D.C. motor

$$V_t = E_b + I_a r_a \times I_a$$

$$I_a V_t = \frac{E_b}{T} I_a + I_a^2 r_a$$

O/P Mechanical Power.

Power = ~~Angular~~ angular speed \times Torque

$$\bullet E_b I_a = \omega T \\ = 2\pi n T$$

$$E_b I_a = 2\pi n T$$

$$\Rightarrow \frac{P \phi N Z}{60 A} \cdot I_a = \frac{2\pi N}{60} \times T$$

$$T = \frac{P \phi Z I_a}{2\pi A} = \frac{P \phi Z I_a}{2\pi A}$$

$$= \left(\frac{PZ}{2\pi A} \right) \phi I_a = K \phi I_a$$


3-phase induction motor

Stator \rightarrow Field

Rotor \rightarrow Armature

Rotating mag. field with a synchronous speed
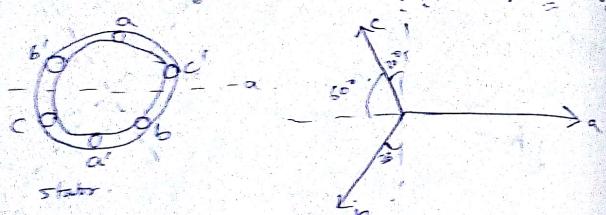
$$\Rightarrow N = \frac{120F}{P} \quad P = 4$$



$$\phi_a = \phi_m \sin \omega t$$

$$\phi_b = \phi_m \sin(\omega t - 120^\circ)$$

$$\phi_c = \phi_m \sin(\omega t - 240^\circ)$$

$$\begin{aligned}\phi_u &= \phi_a - \phi_b \sin 30^\circ - \phi_c \sin 30^\circ \\ &= \phi_m \sin \omega t - \phi_m \sin(\omega t - 120^\circ) \sin 30^\circ - \phi_m \sin(\omega t - 240^\circ) \sin 30^\circ\end{aligned}$$

$$= \phi_m \left[\sin \omega t - (\cos(\omega t - 150^\circ)) \right]$$


~~$$= \cancel{\phi_m \sin \omega t} - \cancel{\phi_m \sin 30^\circ} \cdot \cancel{\frac{1}{2} (\cos(90^\circ - \omega t) - \cos(\omega t - 150^\circ))}$$~~

$$= \phi_m \sin \omega t - \phi_m \sin 30^\circ (2 \sin(\omega t - 30^\circ) \sin 150^\circ)$$

$$= \phi_m \sin \omega t - \phi_m \sin 30^\circ (2 \sin(\omega t - 30^\circ) \sin 150^\circ)$$

$$\begin{aligned}\phi_v &= \phi_c \sin 60^\circ - \phi_b \sin 60^\circ \\ &= \phi_m \sin(\omega t - 240^\circ) \sin 60^\circ - \phi_m \sin(\omega t - 120^\circ) \sin 60^\circ \\ &= \phi_m \sin 60^\circ [\sin(\omega t - 240^\circ) - \sin(\omega t - 120^\circ)] \\ &= \phi_m \sin 60^\circ \cdot 2 \cos(\omega t - 180^\circ) \sin(-60^\circ) \\ &= \frac{3}{2} \phi_m \cos \omega t\end{aligned}$$
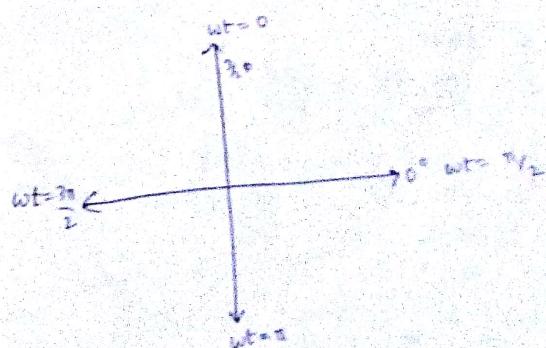
$$\begin{aligned}\phi &= \frac{3}{2} \phi_m L \tan^{-1}(\tan \omega t) \\ &= \frac{3}{2} \phi_m L \tan^{-1}(\tan(\frac{\pi}{3} - \omega t))\end{aligned}$$



N_g = Rotor speed to oppose the main field flux

$$S = \frac{N_s - N_g}{N_s} = \text{slip}$$

$$\begin{aligned} f' &= \text{freq. of em.f induced in rotor} \\ &= s \cdot f \end{aligned}$$

A 4 pole - 3 phase induction machine runs at a speed of 1470 r.p.m. Find out the slip and the frequency of rotor e.m.f.

($f = 50 \text{ Hz}$) if not mentioned.

$$N_s = \frac{120 F}{P}$$

$$N_s = \frac{120 \times 50}{4} = 1500$$

$$\therefore N_g = 1470$$

$$\therefore S = \frac{N_s - N_g}{N_s} = \frac{30}{1500} = \frac{1}{50}$$

$$\therefore f' = \frac{1}{50} \times 50 = 1 \text{ Hz}$$

$$T = \frac{K_1 K_2 E_1 E_2 r_2}{r_2^2 + (s x_2)^2}$$

$$E_1 \propto E_2 \Rightarrow E_1 = K_3 E_2$$

$$\Rightarrow T = \frac{K_1 K_2 (E_1)^2 s r_2}{K_3 (r_2^2 + (s x_2)^2)}$$

$$\Rightarrow T = \frac{K E_1^2 s r_2}{r_2^2 + (s x_2)^2}$$

$$= \frac{3}{\omega_s} \cdot \frac{E_1^2 s r_2}{r_2^2 + (s x_2)^2}$$

On starting $s = 0$ $\therefore N_g = 0$

$$s x_2 \gg r_2$$

$$- T \approx \frac{3}{\omega_s} \frac{E_1^2 s r_2}{s^2 x_2^2}$$

$$\approx \frac{3}{\omega_s} \frac{E_1^2 r_2}{s x_2^2} \approx \frac{3}{\omega_s} \left(\frac{E_1}{r_2} \right)^2 \cdot \frac{r_2}{s}$$


$$T \propto \frac{1}{s}$$

When motor speed is very high

$$s \ll 1$$

$$\therefore T \propto s$$

Torque step characteristic:

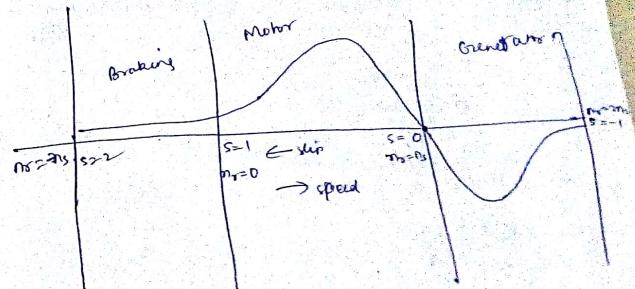

For max-torque

$$E_1 = \text{const}$$

$$T = \frac{K^1 s r_2}{r_2^2 + s^2 x_2^2}$$

$$= \frac{K^1 r_2}{\frac{r_2^2}{s} + s^2 x_2^2}$$

For T to be max^m

$$\frac{r_2^2}{s} + s^2 x_2^2 = \text{should be max}^m$$

$$\frac{d}{ds} \left(\frac{r_2^2}{s} + s^2 x_2^2 \right) = 0$$

$$\Rightarrow -\frac{r_2^2}{s^2} + x_2^2 = 0 \Rightarrow \boxed{x_2 = \frac{s}{r_2}}$$

$$\therefore T = \frac{K^1 s r_2}{2 s x_2^2} = \frac{K^1}{2 x_2^2}$$

$$\therefore T = \frac{3 E_1^2}{2 \omega_s^2 x_2^2}$$

$$\frac{T}{T_{man}} = \frac{2s \cdot s_{man}}{s^2 + s_{man}^2}$$

s_{man} = frequency at which max torque occurs

$$\frac{T_s}{T} = \frac{s^2 + s_{man}^2}{s^2(1+s_{man}^2)}$$

T_s = starting Torque

$$T = \frac{KE_1^2 s r_2}{r_2^2 + (sx_2)^2}$$

$$T_{man} = \frac{KE_1^2}{2x_2}$$

$$\begin{aligned} \frac{T}{T_{man}} &= \frac{2 \frac{KE_1^2 s r_2}{r_2^2 + (sx_2)^2}}{\frac{KE_1^2}{2x_2}} \\ &= \frac{2 s x_2 r_2}{r_2^2 + (sx_2)^2} \\ &= \frac{2 s s_{man} x_2^2}{s_{man}^2 x_2^2 + s^2 x_2^2} \\ &= \frac{2 s s_{man}}{s^2 + s_{man}^2} \end{aligned}$$

alternator coils are thick copper coil

Magnet rotates instead of coils because the ring commutator

Principle of OPM

Cylindrical rotors & Salient/pole rotors

(Assume delta connection if nothing is mentioned)

2 pole machine must rotate at twice the speed of 4 pole m/c to generate same freq.

$$f = N_s \times \frac{P}{2} \times \frac{1}{60}$$

$$\text{Speed} = \sigma \text{ rpm}$$

Open circuit characteristics

$\phi = \text{Flux/Pole}$

$P = \text{No. of poles}$

$N_s = \text{Synchronous}$


form of sine = 1.11 = error/factor

① delta armature \rightarrow delta load
 ② delta " \rightarrow star load

Power & losses

Q types:

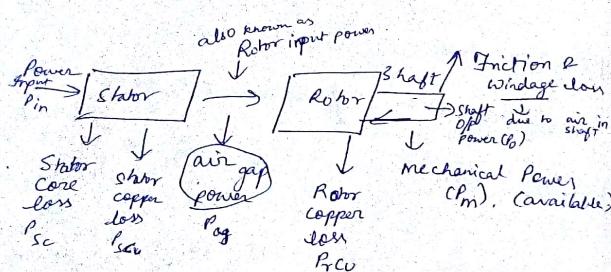- 1) Fixed loss (No load, iron, hysteresis, eddy.)
- 2) Variable loss (air gap)



$$P_{rcu} = s \cdot P_{ag}$$

$$P_m = (1-s) P_{ag} = P_{ag} - P_{rcu}$$

~~Q~~ Rotor output power of 3 phase induction motor is 15 kW, find out the stator copper loss at 4% slip.

$$15 = 0.96 \times P_{ag}$$

$$P_{rcu} = \frac{15}{0.96} \times 0.04 = 0.625 \text{ kW}$$

~~Q~~ A 4 pole 3-phase induction motor is running at 1440 rpm. Rotor input power is 9 kW (or 2 kW)
Find P_{rcu} & P_m

$$N_s = \frac{120 \times 50}{4} = 1500$$

$$N_s = 1440$$

$$s = \frac{N_s - N_r}{N_s} = \frac{1440}{1500} = \frac{4}{100} = 0.04$$

$$P_{rcu} = \frac{0.625 \times 3 \times 1000}{100} = 120 \text{ W}$$

$$P_m = \frac{3000}{3000} - 120 = 2880 \text{ W} \approx 2.88 \text{ kW}$$


Q//


Direct-on-line

Starter of induction motor

Disadvantage

It has very high starting current

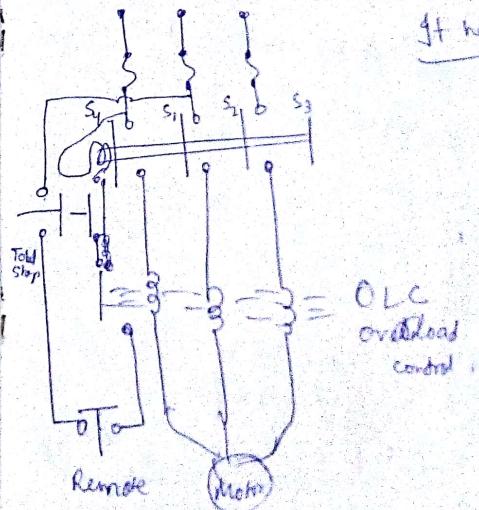

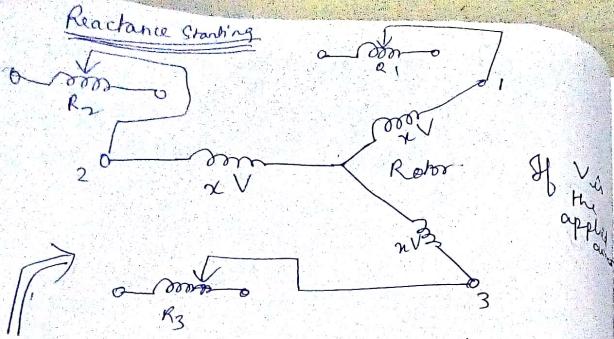

Such an arrangement is provided to vary the reactance dynamically so that initial high current is reduced and later on the reactances R_1, R_2, R_3 can be bypassed.

$$I_{st} = \frac{V}{X} I_{sc} \quad \text{starting current in DOL}$$

Reduction factor $\propto E_1^2$


$$\therefore \propto (\pi V)^2$$

$$T_{st} = I_{st}^2 \frac{\sigma_2}{1}$$

$$T_F = I_{st}^2 \cdot \frac{\sigma_2}{S_{FOL}}$$

$$T = \frac{K \cdot E_1^2 \sigma_2 S}{\sigma_2^2 + (S \sigma_2)^2} = \frac{K E_1^2 S \sigma_2}{S^2 \left(\frac{\sigma_2}{S} \right)^2 + \sigma_2^2}$$
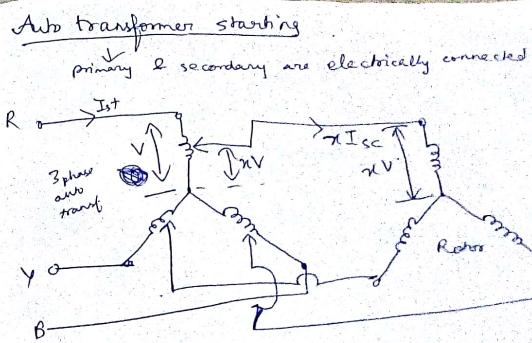
$$= \frac{K E_1^2 \sigma_2}{S \left[\sqrt{\left(\frac{\sigma_2}{S} \right)^2 + 1} \right]^2} = \frac{K I_2^2 \sigma_2}{S}$$



Voltage reduces by $\frac{x}{x+1}$ (per phase value)
Current " "
Torque "

In auto transformer

$$\textcircled{B} \quad V \cdot A \text{mpere} \text{ is const}$$

$$\pi V \cdot \pi I_{sc} = \pi I_{st}$$

$$I_{st} = \pi^2 I_{sc}$$

Star Delta Starting