



Flip Flops and Counters

VLSI Systems
Assignment-7

PREPARED BY

Priyank Lohariwal

BCSE-IV

001710501055

Jadavpur University


Description

Designing flip flops and counters


1. SR Flip Flop
2. 3 bit up counter using SR Flip Flop
 - a. Using component instantiation
 - b. Using behavioral modelling
3. JK Flip Flop
4. 3 bit up counter using JK Flip Flop
 - a. Using component instantiation
 - b. Using behavioural modelling
5. T Flip Flop
6. 3 bit up counter using T Flip Flop
7. 3 bit down counter using T Flip Flop

SR Flip Flop

Block Diagram

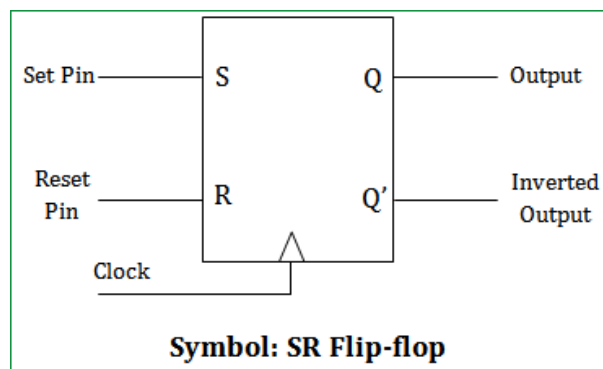

Circuit Diagram

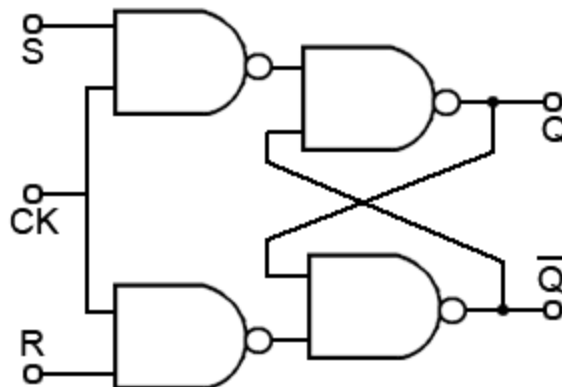

Truth Table

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	x

Code

Implementation

```

architecture Behavioral of srff is
    shared variable q1, notq1: std_logic;
begin
    p1: process(clk, rst)
    begin
        if rst = '1' then
            q <= '0';
            notq <= '1';
            q1 := '0';
            notq1 := '1';
        elsif (clk'event and clk = '1') then
            if (s = '0' and r = '0') then
                q <= q1;
                notq <= notq1;
            elsif (s = '0' and r = '1') then
                q <= '0';
                notq <= '1';
                q1 := '0';
                notq1 := '1';
            elsif (s = '1' and r = '0') then
                q <= '1';
                notq <= '0';
                q1 := '1';
                notq1 := '0';
            else
                q <= 'Z';
                notq <= 'Z';
                q1 := 'Z';
                notq1 := 'Z';
            end if;
        end if;
    end process;
end Behavioral;

```

Test Bench

```
    ARCHITECTURE behavior OF testbench IS

    COMPONENT srff
        Port ( s : in  STD_LOGIC;
              r : in  STD_LOGIC;
              clk : in  STD_LOGIC;
              rst: in  STD_LOGIC;
              q  : out STD_LOGIC;
              notq : out STD_LOGIC);
    END COMPONENT;

    SIGNAL rst : std_logic;
    SIGNAL s : std_logic;
    SIGNAL r : std_logic;
    SIGNAL clk : std_logic;
    SIGNAL q : std_logic;
    SIGNAL notq : std_logic;
BEGIN
-- Component Instantiation
    uut: srff PORT MAP(
        s => s,
        r => r,
        clk => clk,
        rst => rst,
        q => q,
        notq => notq
    );
-- Test Bench Statements
    tb : PROCESS
    BEGIN
        clk <= '0';
        rst <= '0';
        wait for 1ps;

        rst <= '1';
        clk <= '1';
        wait for 1ps;

        rst <= '0';

        loop1: loop
            s <= '0';
```

```

    r <= '0';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;

    s <= '0';
    r <= '1';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;


    s <= '1';
    r <= '0';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;

    s <= '1';
    r <= '1';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;

    end loop;
END PROCESS tb;
END;


```

Timing Diagram

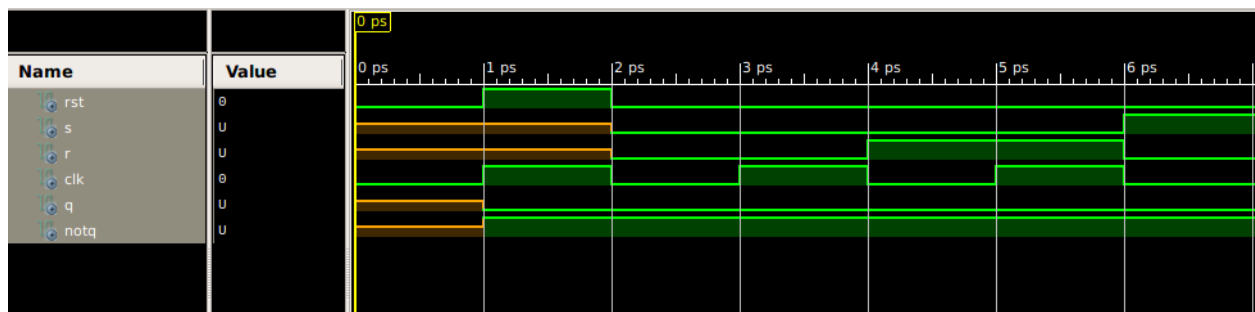


JK Flip Flop

Block Diagram

 

Circuit Diagram

 

Truth Table

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	Q_n'

Code

Implementation

```
architecture Behavioral of jkff is
    shared variable q1, notq1: std_logic;
begin
    p1: process(clk, rst)
        variable temp: std_logic;
    begin
        if rst = '1' then
            q <= '0';
            notq <= '1';
            q1 := '0';
            notq1 := '1';
        elsif (clk'event and clk = '1') then
            if (j = '0' and k = '0') then
                q <= q1;
                notq <= notq1;
            elsif (j = '0' and k = '1') then
                q <= '0';
                notq <= '1';
                q1 := '0';
                notq1 := '1';
            elsif (j = '1' and k = '0') then
                q <= '1';
                notq <= '0';
                q1 := '1';
                notq1 := '0';
            else
                q <= notq;
                notq <= q1;
                temp := q1;
                q1 := notq1;
                notq1 := temp;
            end if;
        end if;
    end process;
end Behavioral;
```

Test Bench

```
ARCHITECTURE behavior OF jkff_test_bench IS
    COMPONENT jkff
    PORT(
        j : IN  std_logic;
        k : IN  std_logic;
        rst : IN  std_logic;
        clk : IN  std_logic;
        q : INOUT std_logic;
        notq : INOUT std_logic
    );
    END COMPONENT;

--Inputs
signal j : std_logic := '0';
signal k : std_logic := '0';
signal rst : std_logic := '0';
signal clk : std_logic := '0';
signal q : std_logic;
signal notq : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: jkff PORT MAP (
        j => j,
        k => k,
        rst => rst,
        clk => clk,
        q => q,
        notq => notq
    );

    -- Stimulus process
    stim_proc: process
    begin
        clk <= '0';
        rst <= '0';
        wait for 1ps;

        rst <= '1';
        clk <= '1';
        wait for 1ps;

        rst <= '0';
```



```

loop1: loop
    j <= '0';
    k <= '0';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;


    j <= '0';
    k <= '1';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;

    j <= '1';
    k <= '0';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;

    j <= '1';
    k <= '1';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;
end loop;
end process;
END;


```

Timing Diagram

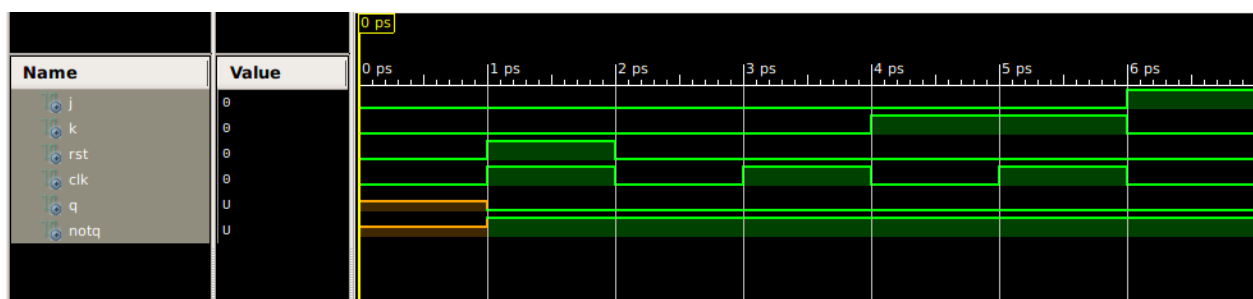


T Flip Flop

Block Diagram

 

Circuit Diagram

 

Truth Table

Q _n	T	Q _{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Code

Implementation

```
architecture Behavioral of tff is
    shared variable q1, notq1: std_logic;
begin
    p1: process(clk, rst)
    begin
        if rst = '1' then
            q <= '0';
            notq <= '1';
            q1 := '0';
            notq1 := '1';
        elsif (clk'event and clk = '1') then
            if t = '0' then
                q <= q1;
                notq <= notq1;
            else
                q <= notq1;
                notq <= q1;
                q1 := notq1;
                notq1 := not q1;
            end if;
        end if;
    end process;
end Behavioral;
```

Test Bench

```
ARCHITECTURE behavior OF tff_test_bench IS
    COMPONENT tff
    PORT(
        t : IN  std_logic;
        rst : IN  std_logic;
        clk : IN  std_logic;
        q : OUT  std_logic;
        notq : OUT  std_logic
    );
    END COMPONENT;

    --Inputs
    signal t : std_logic := '0';
    signal rst : std_logic := '0';
    signal clk : std_logic := '0';

    --Outputs
```

```
signal q : std_logic;
signal notq : std_logic;
BEGIN
-- Instantiate the Unit Under Test (UUT)
 uut: tff PORT MAP (
     t => t,
     rst => rst,
     clk => clk,
     q => q,
     notq => notq
 );
-- Stimulus process
stim_proc: process
begin
  clk <= '0';
  rst <= '0';
  wait for 1ps;


  rst <= '1';
  clk <= '1';
  wait for 1ps;

  rst <= '0';

  loop1: loop
    t <= '0';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;


    t <= '1';
    clk <= '0';
    wait for 1ps;
    clk <= '1';
    wait for 1ps;
  end loop;
end process;
END;
```

Timing Diagram

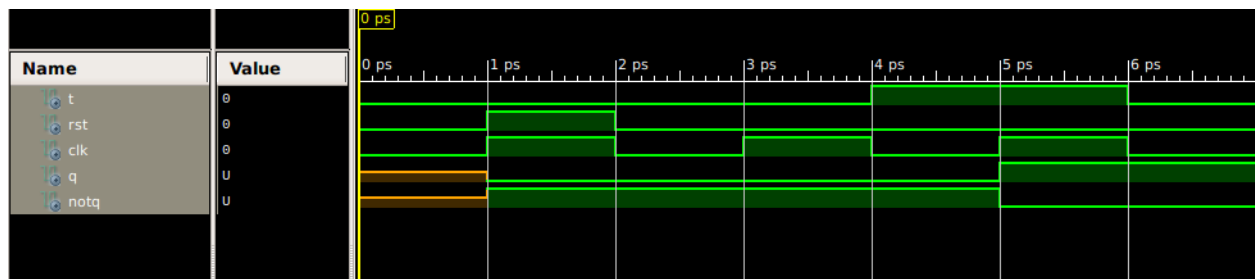


3-bit up counter

Block Diagram

 

Using SR Flip Flops

Circuit Diagram

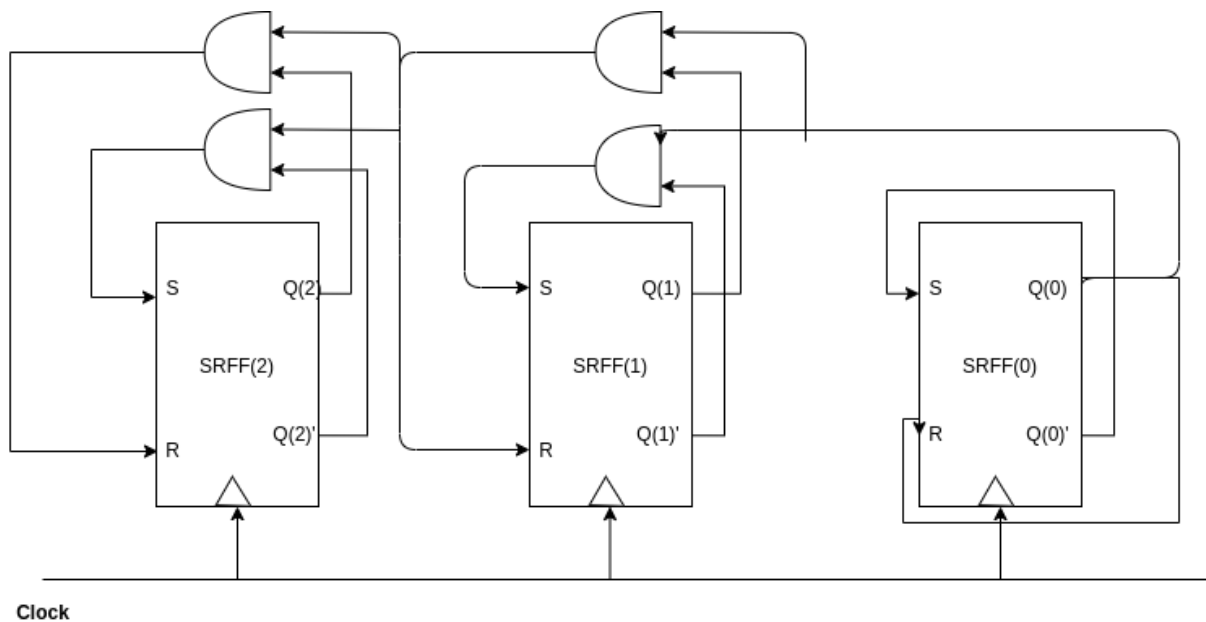

Code


```
architecture Behavioral of counter3bit_a is
    COMPONENT srff
    Port ( s : in  STD_LOGIC;
          r : in  STD_LOGIC;
          clk : in  STD_LOGIC;
          rst: in  STD_LOGIC;
          q : out STD_LOGIC;
          notq : out STD_LOGIC);
    END COMPONENT;
    signal s,r: std_logic_vector(2 downto 0);
begin
    s(2) <= notq(2) and q(1) and q(0);
    r(2) <= q(2) and q(1) and q(0);
    s(1) <= notq(1) and q(0);
    r(1) <= q(1) and q(0);
    s(0) <= notq(0);
    r(0) <= q(0);

    gen1: for k in 0 to 2 generate
        proc: srff port map(s(k), r(k), clk, rst, q(k), notq(k));
    end generate;
end Behavioral;
```

Test Bench


```
ARCHITECTURE behavior OF counter3bit_a_test_bench IS
  COMPONENT counter3bit_a
  PORT(
    rst : IN  std_logic;
    clk : IN  std_logic;
    q : INOUT std_logic_vector(2 downto 0);
    notq : INOUT std_logic_vector(2 downto 0)
  );
  END COMPONENT;
--Inputs
signal rst : std_logic := '0';
signal clk : std_logic := '0';
signal q : std_logic_vector(2 downto 0);
signal notq : std_logic_vector(2 downto 0);
BEGIN
  -- Instantiate the Unit Under Test (UUT)
  uut: counter3bit_a PORT MAP (
    rst => rst,
    clk => clk,
    q => q,
    notq => notq
  );
  -- Stimulus process
  stim_proc: process
  begin
    clk <= '0';
    rst <= '0';
    wait for 1ps;
    rst <= '1';
    clk <= '1';
    wait for 1ps;
    rst <= '0';
    loop1: loop
      clk <= '1';
      wait for 1ps;
      clk <= '0';
      wait for 1ps;
    end loop;
  end process;
END;
```

Timing Diagram

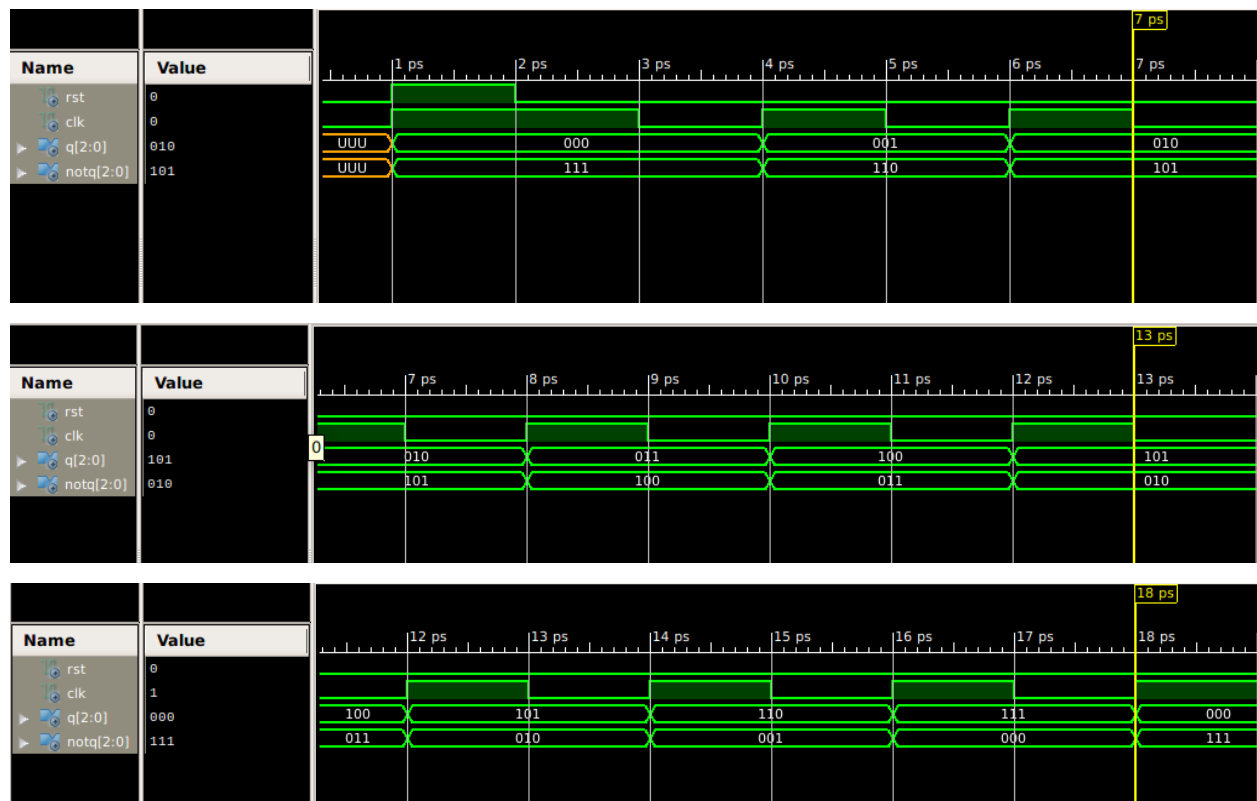

Using JK Flip Flops

Circuit Diagram

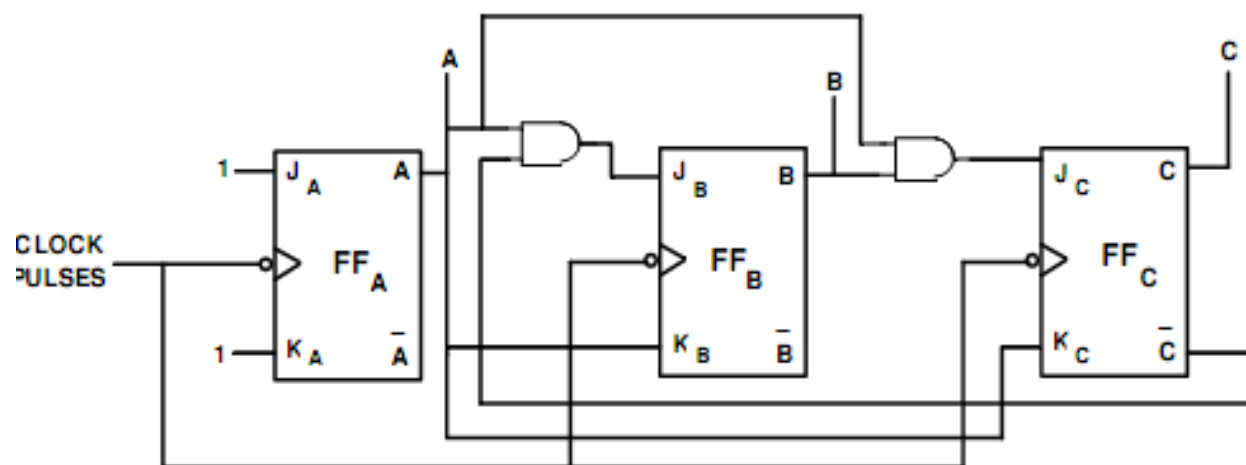

Code

```
architecture Behavioral of counter3bitupjkff is
    COMPONENT jkff
    PORT(
        j : IN  std_logic;
        k : IN  std_logic;
        rst : IN  std_logic;
        clk : IN  std_logic;
        q : INOUT std_logic;
        notq : INOUT std_logic
    );
    END COMPONENT;
    signal j, k: std_logic_vector(2 downto 0);
begin

    j(2) <= q(1) and q(0);
    k(2) <= q(1) and q(0);
    j(1) <= q(0);
    k(1) <= q(0);
    j(0) <= '1';
    k(0) <= '1';

    gen: for i in 0 to 2 generate
        proc: jkff port map(j(i), k(i), rst, clk, q(i), notq(i));
    end generate;

end Behavioral;
```

Test Bench

```
ARCHITECTURE behavior OF counter3bitjkff_test_bench IS
    COMPONENT counter3bitjkff
    PORT(
        rst : IN  std_logic;
        clk : IN  std_logic;
        q : INOUT std_logic_vector(2 downto 0);
        notq : INOUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal rst : std_logic := '0';
    signal clk : std_logic := '0';
```

```
signal q : std_logic_vector(2 downto 0);
signal notq : std_logic_vector(2 downto 0);

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: counter3bitjkff PORT MAP (
    rst => rst,
    clk => clk,
    q => q,
    notq => notq
 );

-- Stimulus process
stim_proc: process
begin

    clk <= '0';
    rst <= '0';
    wait for 1ps;


    rst <= '1';
    clk <= '1';
    wait for 1ps;

    rst <= '0';

    loop1: loop
        clk <= '1';
        wait for 1ps;
        clk <= '0';
        wait for 1ps;
    end loop;
end process;


END;
```

Timing Diagram

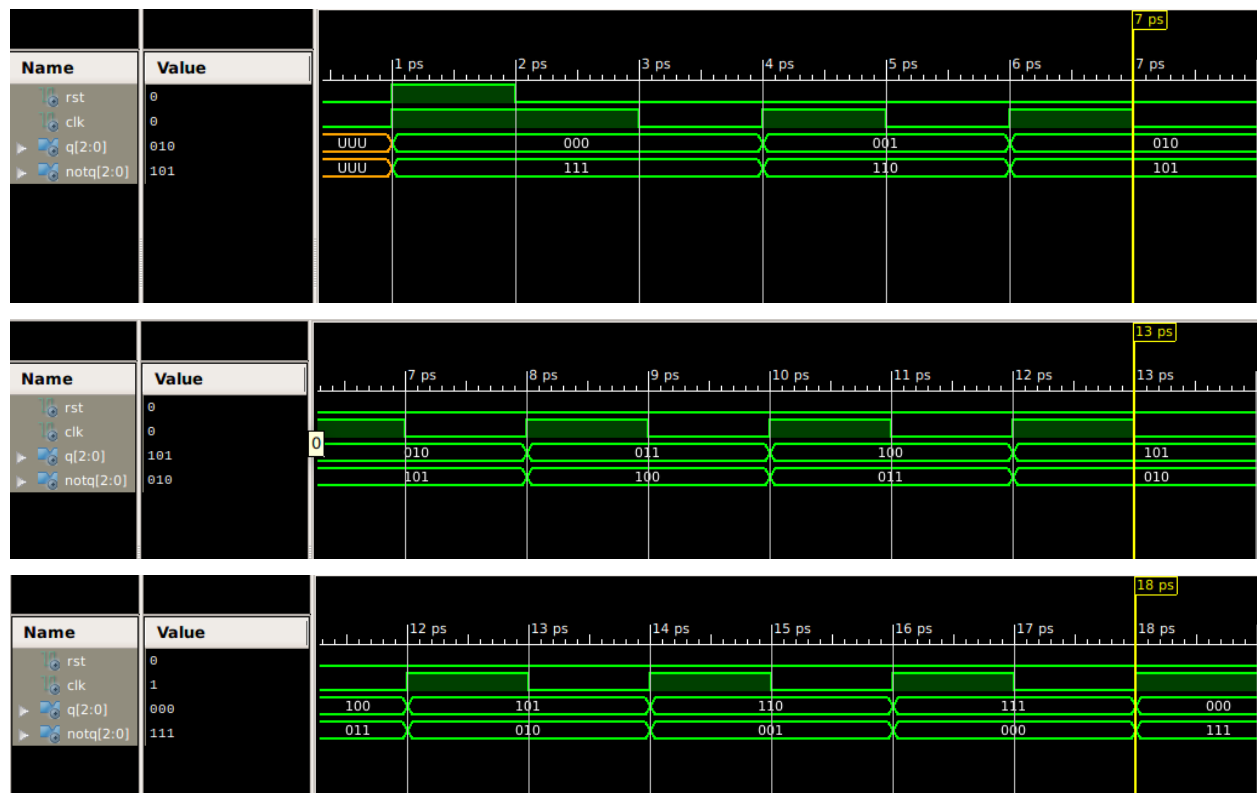

Using T Flip Flops

Circuit Diagram

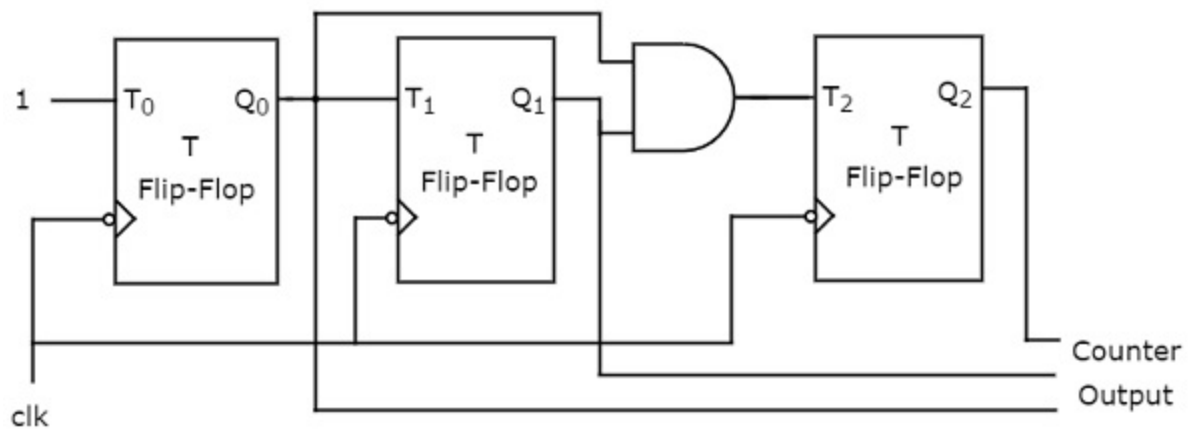

Code

```
architecture Behavioral of counter3bitup_tff is
    COMPONENT tff
    PORT(
        t : IN  std_logic;
        rst : IN  std_logic;
        clk : IN  std_logic;
        q : OUT  std_logic;
        notq : OUT std_logic
    );
    END COMPONENT;

    signal t: std_logic_vector(2 downto 0);
begin
    t(0) <= '1';
    t(1) <= q(0);
    t(2) <= q(0) and q(1);

    gen: for k in 0 to 2 generate
        proc: tff port map(t(k), rst, clk, q(k), notq(k));
    end generate;

end Behavioral;
```

Test Bench

```
ARCHITECTURE behavior OF counter3bitupjkff_test_bench IS

    COMPONENT counter3bitupjkff
    PORT(
        rst : IN  std_logic;
        clk : IN  std_logic;
        q : INOUT std_logic_vector(2 downto 0);
        notq : INOUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal rst : std_logic := '0';
    signal clk : std_logic := '0';

    --BiDirs
```

```
signal q : std_logic_vector(2 downto 0);
signal notq : std_logic_vector(2 downto 0);
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: counter3bitupjkff PORT MAP (
        rst => rst,
        clk => clk,
        q => q,
        notq => notq
    );

    -- Stimulus process
    stim_proc: process
    begin
        clk <= '0';
        rst <= '0';
        wait for 1ps;


        rst <= '1';
        clk <= '1';
        wait for 1ps;

        rst <= '0';

        loop1: loop
            clk <= '0';
            wait for 1ps;
            clk <= '1';
            wait for 1ps;
        end loop;
    end process;


END;
```

Timing Diagram

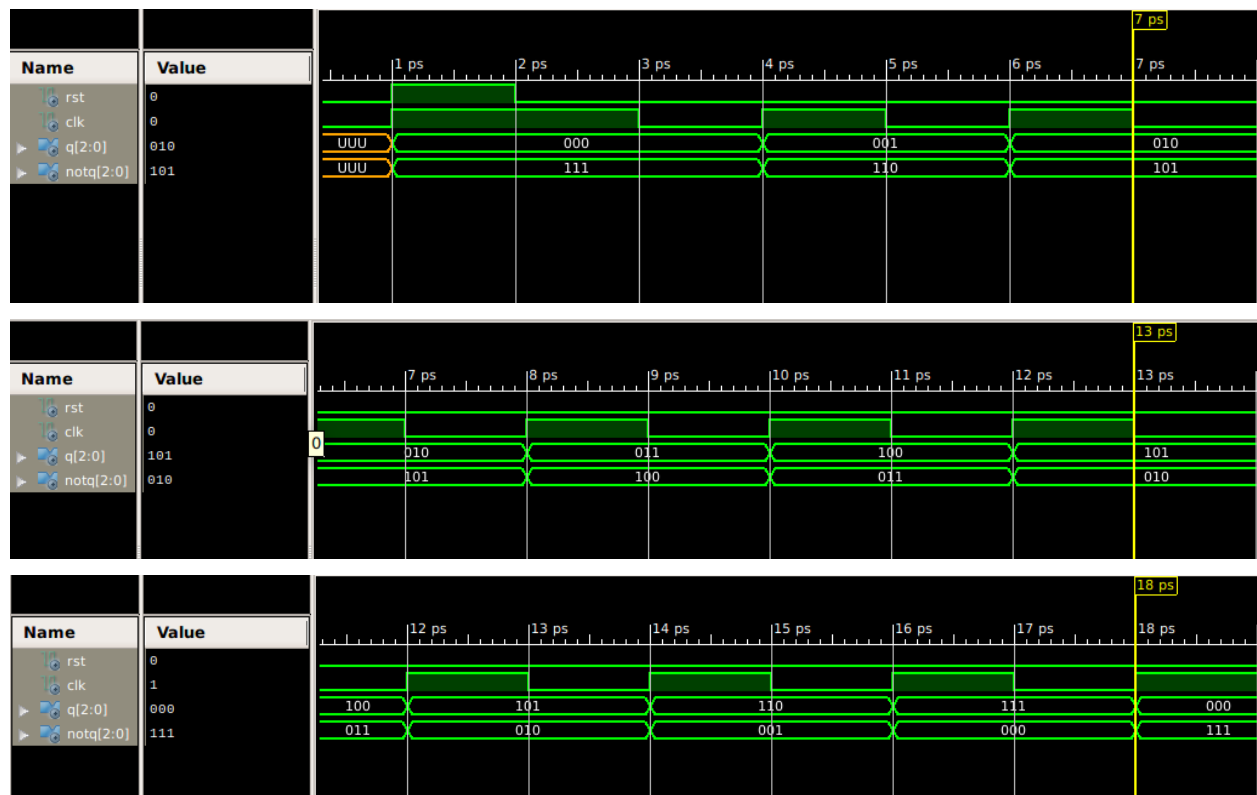


3-bit down counter

Block Diagram

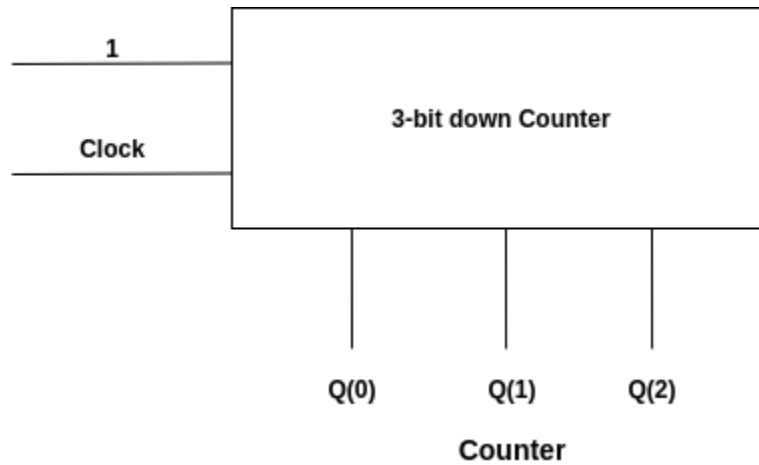

Circuit Diagram

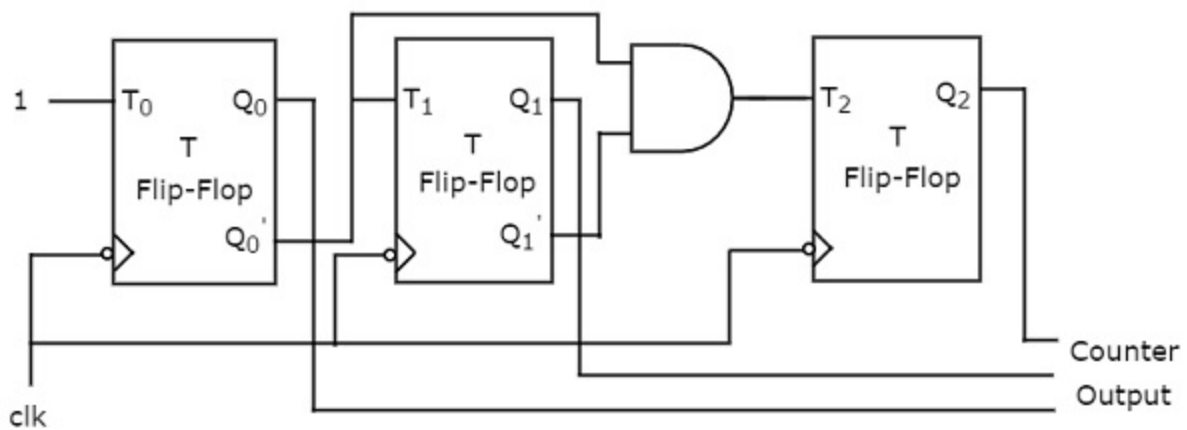

Code

```
architecture Behavioral of counter3bitdown_tff is
    signal t: std_logic_vector(2 downto 0);
    shared variable q1, notq1: std_logic_vector(2 downto 0);
begin
    t(0) <= '1';
    t(1) <= notq(0);
    t(2) <= notq(0) and notq(1);

    gen: for k in 0 to 2 generate
        p1: process(rst, clk)
            begin
```

```

        if rst = '1' then
            q(k) <= '1';
            notq(k) <= '0';
            q1(k) := '1';
            notq1(k) := '0';
        elsif (clk'event and clk = '1') then
            if t(k) = '0' then
                q(k) <= q1(k);
                notq(k) <= notq1(k);
            else
                q(k) <= notq1(k);
                notq(k) <= q1(k);
                q1(k) := notq1(k);
                notq1(k) := not q1(k);
            end if;
        end if;
    end process;
end generate;
end Behavioral;

```

Test Bench

```

ARCHITECTURE behavior OF counter3bitdowntff_test_bench IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT counter3bitdown_tff
    PORT (
        rst : IN  std_logic;
        clk : IN  std_logic;
        q : INOUT std_logic_vector(2 downto 0);
        notq : INOUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal rst : std_logic := '0';
    signal clk : std_logic := '0';

    --Outputs
    signal q : std_logic_vector(2 downto 0);
    signal notq : std_logic_vector(2 downto 0);
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: counter3bitdown_tff PORT MAP (
        rst => rst,
        clk => clk,
        q => q,

```



```

        notq => notq
    );
-- Stimulus process
stim_proc: process
begin
    rst <= '0';
    clk <= '0';
    wait for 1ps;
    rst <= '1';
    clk <= '1';
    wait for 1ps;
    rst <= '0';
    loop1: loop
        clk <= '0';
        wait for 1ps;
        clk <= '1';
        wait for 1ps;
    end loop;
end process;
END;

```

Timing Diagram

